

Figura 4: Máquina de estados do *Key Control*

 


Figura 5: Diagrama de Blocos do *Key Control*

2 Ring Buffer

O bloco *Ring Buffer* foi implementado de acordo com o diagrama de blocos representado na Figura 6. O *Ring Buffer* tem como objetivo controlar a entrada de teclas vinda do *Key Decoder* através do *Ring Buffer Control* e com o *Memory Address Control* gerenciar o acesso à *RAM* para poder guardar as mesmas. Com isso, usando como referência o diagrama de blocos da Figura 6, a nossa implementação está representada na Figura 7.

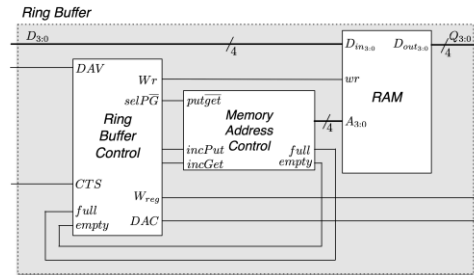


Figura 6: Diagrama de Blocos do *Ring Buffer*

 


Figura 7: Diagrama de Blocos do módulo *Ring Buffer*

2.1 Ring Buffer Control

O *Ring Buffer Control* como dito anteriormente, tem a função de controlar as entrada das teclas vindas do *Key Decoder* e ao mesmo tempo gerenciar se a *RAM* tem espaço para armazenar essas teclas ou não. Com isso para a conceção do mesmo foi implementado pela máquina de estados representada pelo ASM-chart da figura 8. A máquina de estados consiste em 2 fases onde quando houver dados (DAV) e a *RAM* não estiver cheia, as teclas serão escritas e quando os dados estiverem prontos para serem enviados para o *Output Buffer* (CTS) e a *RAM* não estiver vazia irá ler os mesmos. O diagrama de blocos que representa o *Ring Buffer Control* está representado na 9.

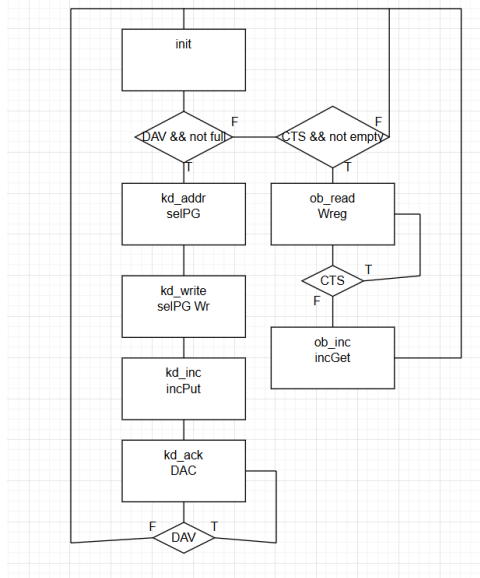


Figura 8: ASM-Chart do *Ring Buffer Control*

 


Figura 9: Diagrama de Blocos do módulo *Ring Buffer Control*

2.2 Memory Address Control

O bloco Memory Address Control é o responsável por gerenciar o acesso de escrita e leitura à RAM assim, manipulando o endereço onde irá escrever e de onde irá ler. Além, disso ainda informa ao *Ring Buffer Control* quando a RAM está vazia ou cheia. Com isso para a implementação do *Memory Address Control* foram usados 2 *Counters* de 4 bits onde a ativação dos mesmos é controlado pelos sinais incPut e incGet no qual, a saída de cada um destes *Counters* resulta como entrada do *Mu4-MAC* que é ativado pelo sinal putget e a saída é o address da RAM. Por fim, ainda temos um *Registro* que incrementa o putget sempre que houver incGet ou incPut e a saída gerencia quando que a RAM está cheia ou vazia. O diagrama de blocos que representa o *Memory Address Control* está

representado na 10.

 


Figura 10: Diagrama de Blocos do módulo *Memory Address Control*

2.3 RAM

O bloco RAM já é fornecido pelos professores no qual, através dele é possível armazenar as teclas e consultar as mesmas quando necessário. O diagrama de blocos que representa o RAM está representado na 11.

 


Figura 11: Diagrama de Blocos do módulo *RAM*

3 Output Buffer

O *Output Buffer* é o último bloco no Hardware antes de enviar os dados para o *Control*. Assim, o *Output Buffer* é constituído por outros 2 blocos *Buffer Control* e *Output Register* e a função do bloco como um todo é perceber quando que os dados estão disponíveis para serem recebidos do bloco *Ring Buffer* para os enviar para o bloco *Control*. Então com base no diagrama de bloco da Figura 12 implementámos a nossa versão do mesmo estando disponível o diagrama de blocos na Figura 13.

3.1 Buffer Control

O *Buffer Control* faz o manuseamento de quando os dados são enviados para o controlo assim, para a implementação do mesmo recorreremos a uma máquina de estados representada por um ASM-char na Figura 14. Quando o *Buffer Control* estiver

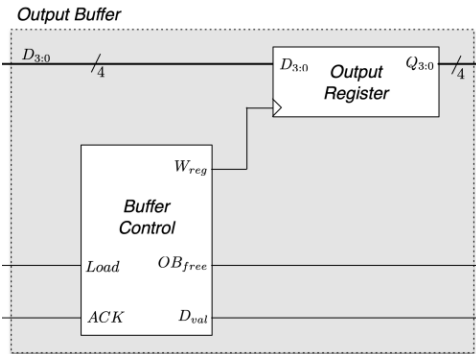


Figura 12: Diagrama de Blocos do *Output Buffer*

 


Figura 13: Diagrama de Blocos do módulo *Output Buffer*

disponível para receber dados(OBfree) e o *Ring Buffer* informar que tem dados(Load) irá ativar o clock do *Output Register* para receber e enviar os dados e de seguida irá informar ao *Control* que os dados são válidos(Dval) e depois espera pela confirmação do *Control* que recebeu os dados(Ack) para voltar a estar disponível para receber dados. Assim o resultado da nossa implementação está disponível no diagrama de blocos da Figura 15.

3.2 Output Register

O *Output Register* é apenas responsável por guardar os dados provenientes do *Ring Buffer* e enviar para o *Control*. Sendo assim o *Output Register* é apenas um componente que detém de 4 FFD's onde cada um guarda o seu bit e envia. Com isto o diagrama de blocos do *Output Register* está disponível na Figura 16. O componente usado para o *Output Register* foi o A.11.

4 Keyboard Reader

O *Keyboard Reader* é o módulo que recebe as teclas, processa as mesmas e eventualmente envia

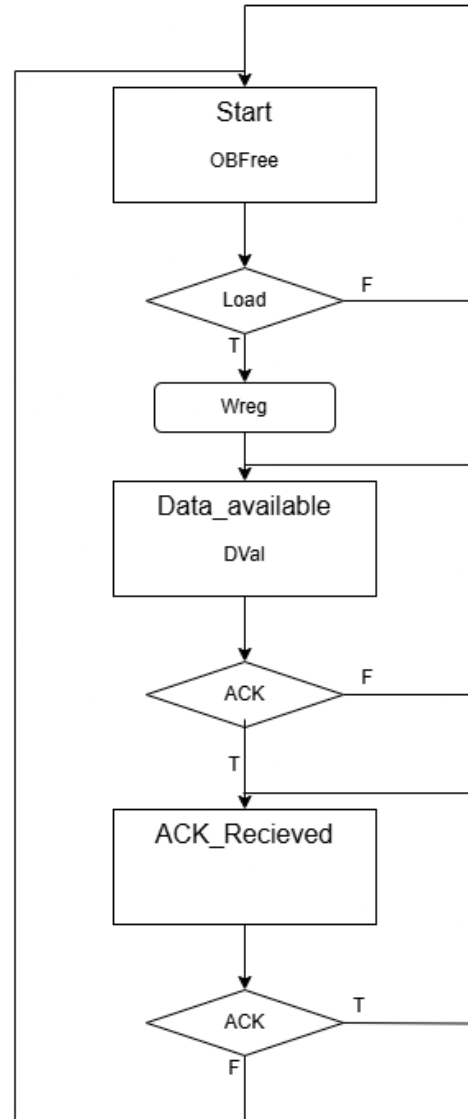


Figura 14: ASM do *Buffer Control*

 


Figura 15: Diagrama de Blocos do módulo *Buffer Control*

para o *Control*. Dentro do *Keyboard Reader* temos o *Key Decode* que controla a deteção de teclas pres-

 


Figura 16: Diagrama de Blocos do módulo *Output Register*

sionadas e as envia para o *Ring Buffer* que guarda estas mesmas teclas numa *Ram* e envia para o *Output Buffer* que este é responsável por fazer a ligação com o *Control* enviando as teclas para o mesmo. Assim, sendo o diagrama de blocos do *Keyboard Reader* está disponível na Figura 17.

 


Figura 17: Diagrama de Blocos do módulo *Keyboard Reader*

5 Conclusões

Na conclusão deste módulo do trabalho, conseguimos processar e decodificar *inputs* do teclado, e enviar para o *software* através dos módulos *Key Decode*, *Ring Buffer* e *Output Buffer*. Apesar de em geral ter o funcionamento esperado, deparamo-nos com um erro durante o processo de leitura das teclas. O erro em questão causava que, durante o processo de leitura da tecla, os inputs eram processados muito mais do que uma vez, causando a ilusão de que a tecla estava a ser carregada repetidas vezes, ao invés de apenas uma.

A VHDL

A.1 Roleta

```
library ieee;
use ieee.std_logic_1164.all;

entity Roleta is
  port(

    -- input
    CLK: in std_logic;
    Reset: in std_logic;
    KBD_KeyLin: in std_logic_vector(3 downto 0);
    Coin: in std_logic;
    CoinID: in std_logic;
    Maintenance_in: in std_logic;

    -- output
    KBD_KeyCol: out std_logic_vector(3 downto 0);
    LCD_E: out std_logic;
    LCD_RS: out std_logic;
    LCD_D: out std_logic_vector(7 downto 0);
    RD_HEX0: out std_logic_vector(7 downto 0);
    RD_HEX1: out std_logic_vector(7 downto 0);
    RD_HEX2: out std_logic_vector(7 downto 0);
    RD_HEX3: out std_logic_vector(7 downto 0);
    RD_HEX4: out std_logic_vector(7 downto 0);
    RD_HEX5: out std_logic_vector(7 downto 0);
    Accept: out std_logic;

    debug_full: out std_logic;
    debug_empty: out std_logic

  );
end Roleta;

architecture logicFunction of Roleta is

  component UsbPort is
    port(

      -- input
      inputPort: in std_logic_vector(7 downto 0);

      -- output
      outputPort: out std_logic_vector(7 DOWNT0 0)

    );
  end component;

  component KeyboardReader is
    port(

      -- input
      KeyboardReader_Ack: in std_logic;
      KeyboardReader_Lin: in std_logic_vector(3 downto 0);
      KeyboardReader_CLK: in std_logic;
      KeyboardReader_Reset: in std_logic;

      -- output
      KeyboardReader_Col: out std_logic_vector(3 downto 0);
```



ISEL

Departamento de Engenharia
Eletrónica e Telecomunicações
e de Computadores

Keyboard Decode (*Roulette Game*)

Laboratório de Informática e Computadores 2024 / 2025 verão

Autores: Ricardo Martins nº52326 / Bernardo Silva nº52605 / Bernardo Esteves nº52948

```
KeyboardReader_Dval: out std_logic;
KeyboardReader_Q: out std_logic_vector(3 downto 0);

debug_full: out std_logic;
debug_empty: out std_logic

);
end component;

component SLCDC is
port(

    -- input
    SLCDC_Reset: in std_logic;
    SLCDC_LCDSel: in std_logic;
    SLCDC_SCLK: in std_logic;
    SLCDC_CLK: in std_logic;
    SLCDC_SDx: in std_logic;

    -- output
    SLCDC_E: out std_logic;
    SLCDC_D: out std_logic_vector(4 downto 0)

);
end component;

component SRC is
port(

    -- input
    SRC_Reset: in std_logic;
    SRC_RDSel: in std_logic;
    SRC_SCLK: in std_logic;
    SRC_CLK: in std_logic;
    SRC_SDx: in std_logic;

    -- output
    SRC_set: out std_logic;
    SRC_D: out std_logic_vector(7 downto 0)

);
end component;

component rouletteDisplay is
port(

    -- input
    set: in std_logic;
    cmd: in std_logic_vector(2 downto 0);
    data: in std_logic_vector(4 downto 0);

    -- output
    HEX0: out std_logic_vector(7 downto 0);
    HEX1: out std_logic_vector(7 downto 0);
    HEX2: out std_logic_vector(7 downto 0);
    HEX3: out std_logic_vector(7 downto 0);
    HEX4: out std_logic_vector(7 downto 0);
    HEX5: out std_logic_vector(7 downto 0)

);
end component;

component CoinAcceptor is
```

```

port(

    -- input
    CoinAcceptor_Accept_in: in std_logic;
    CoinAcceptor_Coin_in: in std_logic;
    CoinAcceptor_CoinID_in: in std_logic;

    -- output
    CoinAcceptor_Accept_out: out std_logic;
    CoinAcceptor_Coin_out: out std_logic;
    CoinAcceptor_CoinID_out: out std_logic

);
end component;

component Maintenance is
port(

    -- input
    Maintenance_in: in std_logic;

    -- output
    Maintenance_out: out std_logic

);
end component;

-- Input (Hardware → Software)
signal usb_input: std_logic_vector(7 downto 0);

-- Output (Software → Hardware)
signal usb_output: std_logic_vector(7 downto 0);

signal RD_set: std_logic;
signal RD_cmd: std_logic_vector(2 downto 0);
signal RD_data: std_logic_vector(4 downto 0);

-- signal tmp: std_logic_vector(9 downto 0);

begin

u0: UsbPort port map (
    inputPort => usb_input,
    outputPort => usb_output
);

u1: KeyboardReader port map (
    KeyboardReader_Ack => usb_output(7),
    KeyboardReader_Lin => KBD_KeyLin,
    KeyboardReader_CLK => CLK,
    KeyboardReader_Reset => Reset,
    KeyboardReader_Col => KBD_KeyCol,
    KeyboardReader_Dval => usb_input(4),
    KeyboardReader_Q => usb_input(3 downto 0),
    debug_empty => debug_empty,
    debug_full => debug_full
);

u2: SLCDC port map (
    SLCDC_Reset => Reset,
    SLCDC_LCDSel => usb_output(0),

```



```
SLCDC_SCLK => usb_output(4),
SLCDC_CLK => CLK,
SLCDC_SDx => usb_output(3),
SLCDC_E => LCD_E,
SLCDC_D(0) => LCD_RS,
SLCDC_D(4 downto 1) => LCD_D(7 downto 4)
);

u3: SRC port map (
  SRC_Reset => Reset,
  SRC_RDsel => usb_output(1),
  SRC_SCLK => usb_output(4),
  SRC_CLK => CLK,
  SRC_SDx => usb_output(3),
  SRC_set => RD_set,
  SRC_D(2 downto 0) => RD_cmd,
  SRC_D(7 downto 3) => RD_data
);

u4: rouletteDisplay port map (
  set => RD_set,
  cmd => RD_cmd,
  data => RD_data,
  HEX0 => RD_HEX0,
  HEX1 => RD_HEX1,
  HEX2 => RD_HEX2,
  HEX3 => RD_HEX3,
  HEX4 => RD_HEX4,
  HEX5 => RD_HEX5
);

u5: CoinAcceptor port map (
  CoinAcceptor_Accept_in => usb_output(6),
  CoinAcceptor_Coin_in => Coin,
  CoinAcceptor_CoinID_in => CoinID,
  CoinAcceptor_Accept_out => Accept,
  CoinAcceptor_Coin_out => usb_input(6),
  CoinAcceptor_CoinID_out => usb_input(5)
);

u6: Maintenance port map (
  Maintenance_in => Maintenance_in,
  Maintenance_out => usb_input(7)
);

end logicFunction;
```

A.2 UsbPort

```
-- Copyright (C) 2020 Intel Corporation. All rights reserved.
-- Your use of Intel Corporation's design tools, logic functions
-- and other software and tools, and any partner logic
-- functions, and any output files from any of the foregoing
-- (including device programming or simulation files), and any
-- associated documentation or information are expressly subject
-- to the terms and conditions of the Intel Program License
-- Subscription Agreement, the Intel Quartus Prime License Agreement,
-- the Intel FPGA IP License Agreement, or other applicable license
-- agreement, including, without limitation, that your use is for
-- the sole purpose of programming logic devices manufactured by
-- Intel and sold by Intel or its authorized distributors. Please
-- refer to the applicable agreement for further details, at
-- https://fpgasoftware.intel.com/eula.

-- PROGRAM          "Quartus Prime"
-- VERSION           "Version 20.1.1 Build 720 11/11/2020 SJ Lite Edition"
-- CREATED           "Tue Mar 01 09:42:31 2022"

library ieee;
use ieee.std_logic_1164.all;

library work;

entity UsbPort is
    port(
        inputPort: in std_logic_vector(7 downto 0);
        outputPort: out std_logic_vector(7 downto 0)
    );
end UsbPort;

architecture bdf_type of UsbPort is

    component sld_virtual_jtag
        GENERIC(
            lpm_type: string;
            sld_auto_instance_index: string;
            sld_instance_index: integer;
            sld_ir_width: integer;
            sld_sim_action: string;
            sld_sim_n_scan: integer;
            sld_sim_total_length: integer
        );
    PORT(
        tdo: in std_logic;
        ir_out: in std_logic_vector(7 downto 0);
        tck: out std_logic;
        tdi: out std_logic;
        virtual_state_cdr: out std_logic;
        virtual_state_sdr: out std_logic;
        virtual_state_e1dr: out std_logic;
        virtual_state_pdr: out std_logic;
        virtual_state_e2dr: out std_logic;
        virtual_state_uds: out std_logic;
        virtual_state_cir: out std_logic;
        virtual_state_uir: out std_logic;
        tms: out std_logic;
        jtag_state_tlr: out std_logic;
        jtag_state_rti: out std_logic;
        jtag_state_sdrs: out std_logic;
        jtag_state_cdr: out std_logic;
```



ISEL

Departamento de Engenharia
Eletrónica e Telecomunicações
e de Computadores

Keyboard Decode (*Roulette Game*)

Laboratório de Informática e Computadores 2024 / 2025 verão

Autores: Ricardo Martins nº52326 / Bernardo Silva nº52605 / Bernardo Esteves nº52948

```
jtag_state_sdr: out std_logic;
jtag_state_e1dr: out std_logic;
jtag_state_pdr: out std_logic;
jtag_state_e2dr: out std_logic;
jtag_state_udr: out std_logic;
jtag_state_sirs: out std_logic;
jtag_state_cir: out std_logic;
jtag_state_sir: out std_logic;
jtag_state_e1ir: out std_logic;
jtag_state_pir: out std_logic;
jtag_state_e2ir: out std_logic;
jtag_state_uir: out std_logic;
ir_in: out std_logic_vector(7 downto 0)

);
end component;

begin

b2v_inst: sld_virtual_jtag
  generic map (
    lpm_type => "sld_virtual_jtag",
    sld_auto_instance_index => "YES",
    sld_instance_index => 0,
    sld_ir_width => 8,
    sld_sim_action => "UNUSED",
    sld_sim_n_scan => 0,
    sld_sim_total_length => 0
  )
  port map (
    ir_out => inputPort,
    ir_in => outputPort
  );

end bdf_type;
```

A.3 KeyBoard Reader

```
library ieee;
use ieee.std_logic_1164.all;

entity KeyboardReader is
    port(

        -- input
        KeyboardReader_Ack: in std_logic;
        KeyboardReader_Lin: in std_logic_vector(3 downto 0);
        KeyboardReader_CLK: in std_logic;
        KeyboardReader_Reset: in std_logic;

        -- output
        KeyboardReader_Col: out std_logic_vector(3 downto 0);
        KeyboardReader_Dval: out std_logic;
        KeyboardReader_Q: out std_logic_vector(3 downto 0);

        debug_full: out std_logic;
        debug_empty: out std_logic

    );
end KeyboardReader;

architecture logicFunction of KeyboardReader is

    component KeyDecode is
        port(

            -- input
            KeyDecode_Ack: in std_logic;
            KeyDecode_Lin: in std_logic_vector(3 downto 0);
            KeyDecode_CLK: in std_logic;
            KeyDecode_Reset: in std_logic;

            -- output
            KeyDecode_Col: out std_logic_vector(3 downto 0);
            KeyDecode_Val: out std_logic;
            KeyDecode_K: out std_logic_vector(3 downto 0)

        );
    end component;

    component RingBuffer is
        port(

            -- input
            RingBuffer_D: in std_logic_vector(3 downto 0);
            RingBuffer_DAV: in std_logic;
            RingBuffer_CLK: in std_logic;
            RingBuffer_Reset: in std_logic;
            RingBuffer_CTS: in std_logic;

            -- output
            RingBuffer_Q: out std_logic_vector(3 downto 0);
            RingBuffer_Wreg: out std_logic;
            RingBuffer_DAC: out std_logic;

            debug_full: out std_logic;
            debug_empty: out std_logic

        );
    end component;
```

```

end component;

component OutputBuffer is
  port(

    -- input
    OutputBuffer_D: in std_logic_vector(3 downto 0);
    OutputBuffer_Load: in std_logic;
    OutputBuffer_ACK: in std_logic;
    OutputBuffer_Reset: in std_logic;
    OutputBuffer_CLK: in std_logic;

    -- output
    OutputBuffer_Q: out std_logic_vector(3 downto 0);
    OutputBuffer_OBfree: out std_logic;
    OutputBuffer_Dval: out std_logic

  );
end component;

signal K_to_D: std_logic_vector(3 downto 0);
signal Q_to_D: std_logic_vector(3 downto 0);
signal DAC_to_Kack: std_logic;
signal Kval_to_DAV: std_logic;
signal OBfree_to_CTS: std_logic;
signal Wreg_to_Load: std_logic;

begin

u0: KeyDecode port map (
  KeyDecode_CLK => KeyboardReader_CLK,
  KeyDecode_Reset => KeyboardReader_Reset,
  KeyDecode_Lin => KeyboardReader_Lin,
  KeyDecode_Ack => DAC_to_Kack,
  KeyDecode_Col => KeyboardReader_Col,
  KeyDecode_Val => Kval_to_DAV,
  KeyDecode_K => K_to_D
);

u1: RingBuffer port map (
  RingBuffer_D => K_to_D,
  RingBuffer_DAV => Kval_to_DAV,
  RingBuffer_CLK => KeyboardReader_CLK,
  RingBuffer_Reset => KeyboardReader_Reset,
  RingBuffer_CTS => OBfree_to_CTS,
  RingBuffer_Q => Q_to_D,
  RingBuffer_Wreg => Wreg_to_Load,
  RingBuffer_DAC => DAC_to_Kack,

  debug_empty => debug_empty,
  debug_full => debug_full
);

u2: OutputBuffer port map (
  OutputBuffer_D => Q_to_D,
  OutputBuffer_Load => Wreg_to_Load,
  OutputBuffer_ACK => KeyboardReader_Ack,
  OutputBuffer_Reset => KeyboardReader_Reset,
  OutputBuffer_CLK => KeyboardReader_CLK,
  OutputBuffer_Q => KeyboardReader_Q,
  OutputBuffer_OBfree => OBfree_to_CTS,
  OutputBuffer_Dval => KeyboardReader_Dval

```

```
);
```

```
end logicFunction;
```

A.4 KeyBoard Decoder

```
library ieee;
use ieee.std_logic_1164.all;

entity KeyDecode is
    port(

        -- input
        KeyDecode_Ack: in std_logic;
        KeyDecode_Lin: in std_logic_vector(3 downto 0);
        KeyDecode_CLK: in std_logic;
        KeyDecode_Reset: in std_logic;

        -- output
        KeyDecode_Col: out std_logic_vector(3 downto 0);
        KeyDecode_Val: out std_logic;
        KeyDecode_K: out std_logic_vector(3 downto 0)
    );
end KeyDecode;

architecture logicFunction of KeyDecode is

    component KeyScan is
        port(

            -- input
            KeyScan_Lin: in std_logic_vector(3 downto 0);
            KeyScan_Scan: in std_logic;
            KeyScan_CLK: in std_logic;
            KeyScan_Reset: in std_logic;

            -- output
            KeyScan_Col: out std_logic_vector(3 downto 0);
            KeyScan_K: out std_logic_vector(3 downto 0);
            KeyScan_Press: out std_logic
        );
    end component;

    component KeyControl is
        port(

            -- input
            KeyControl_Ack: in std_logic;
            KeyControl_Press: in std_logic;
            KeyControl_CLK: in std_logic;
            KeyControl_Reset: in std_logic;

            -- output
            KeyControl_Val: out std_logic;
            KeyControl_Scan: out std_logic
        );
    end component;

    component ClkDiv is
        port(
            -- input
            clk_in: in std_logic;

            -- output
            clk_out: out std_logic
        );
    end component;
```

```
    );  
end component;  
  
signal Scan: std_logic;  
signal Press: std_logic;  
signal clk: std_logic;  
  
begin  
  
    u0: KeyScan port map (  
        KeyScan_Lin => KeyDecode_Lin,  
        KeyScan_Scan => Scan,  
        KeyScan_CLK => clk,  
        KeyScan_Reset => KeyDecode_Reset,  
        KeyScan_Col => KeyDecode_Col,  
        KeyScan_K => KeyDecode_K,  
        KeyScan_Press => Press  
    );  
  
    u1: KeyControl port map (  
        KeyControl_Ack => KeyDecode_Ack,  
        KeyControl_Press => Press,  
        KeyControl_CLK => clk,  
        KeyControl_Reset => KeyDecode_Reset,  
        KeyControl_Val => KeyDecode_Val,  
        KeyControl_Scan => Scan  
    );  
  
    u2: ClkDiv port map (  
        clk_in => KeyDecode_CLK,  
        clk_out => clk  
    );  
  
end logicFunction;
```


A.5 KeyBoard Scan

```
library ieee;
use ieee.std_logic_1164.all;

entity KeyScan is
    port(

        -- input
        KeyScan_Lin: in std_logic_vector(3 downto 0);
        KeyScan_Scan: in std_logic;
        KeyScan_CLK: in std_logic;
        KeyScan_Reset: in std_logic;

        -- output
        KeyScan_Col: out std_logic_vector(3 downto 0);
        KeyScan_K: out std_logic_vector(3 downto 0);
        KeyScan_Press: out std_logic

    );
end KeyScan;

architecture logicFunction of KeyScan is

    component Counter4 is
        port(

            -- input
            Counter4_CE: in std_logic;
            Counter4_CLK: in std_logic;
            Counter4_Reset: in std_logic;

            -- output
            Counter4_Q: out std_logic_vector(3 downto 0)

        );
    end component;

    component Dec4 is
        port(

            -- input
            Dec4_S: in std_logic_vector(1 downto 0);

            -- output
            Dec4_Out: out std_logic_vector(3 downto 0)

        );
    end component;

    component Mux4 is
        port(

            -- input
            Mux4_In: in std_logic_vector(3 downto 0);
            Mux4_S: in std_logic_vector(1 downto 0);

            -- output
            Mux4_Out: out std_logic

        );
    end component;
```

```
signal Q: std_logic_vector(3 downto 0);
signal Not_KeyScan_Col: std_logic_vector(3 downto 0);
signal Not_KeyScan_Press: std_logic;

begin

    u0: Counter4 port map (
        Counter4_CE => KeyScan_Scan,
        Counter4_CLK => KeyScan_CLK,
        Counter4_Reset => KeyScan_Reset,
        Counter4_Q => Q
    );

    KeyScan_K <= Q;

    u1: Dec4 port map (
        Dec4_S(1) => Q(3),
        Dec4_S(0) => Q(2),
        Dec4_Out => Not_KeyScan_Col
    );

    KeyScan_Col(3) <= not Not_KeyScan_Col(3);
    KeyScan_Col(2) <= not Not_KeyScan_Col(2);
    KeyScan_Col(1) <= not Not_KeyScan_Col(1);
    KeyScan_Col(0) <= not Not_KeyScan_Col(0);

    u2: Mux4 port map (
        Mux4_In => KeyScan_Lin,
        Mux4_S(1) => Q(1),
        Mux4_S(0) => Q(0),
        Mux4_Out => Not_KeyScan_Press
    );

    KeyScan_Press <= not Not_KeyScan_Press;

end logicFunction;
```

A.6 KeyBoard Control

```
library ieee;
use ieee.std_logic_1164.all;

entity KeyControl is
    port(

        -- input
        KeyControl_Ack: in std_logic;
        KeyControl_Press: in std_logic;
        KeyControl_CLK: in std_logic;
        KeyControl_Reset: in std_logic;

        -- output
        KeyControl_Val: out std_logic;
        KeyControl_Scan: out std_logic

    );
end KeyControl;

architecture logicFunction of KeyControl is

    type Tstate is (scanning, hold, resume);

    signal state: Tstate;
    signal next_state: Tstate;

begin

    state <= scanning when KeyControl_Reset = '1' else next_state when falling_edge(KeyControl_CLK);

    process(state, KeyControl_Ack, KeyControl_Press) begin
        case state is

            when scanning =>
                if KeyControl_Press = '1' then
                    next_state <= hold;
                else
                    next_state <= scanning;
                end if;

            when hold =>
                if KeyControl_Ack = '1' then
                    next_state <= resume;
                else
                    next_state <= hold;
                end if;

            when resume =>
                if KeyControl_Ack = '0' and KeyControl_Press = '0' then
                    next_state <= scanning;
                else
                    next_state <= resume;
                end if;

        end case;
    end process;

    KeyControl_Val <= '1' when state = hold else '0';
    KeyControl_Scan <= '1' when state = scanning and KeyControl_Press = '0' else '0';

end logicFunction;
```

A.7 Decoder

```
library ieee;
use ieee.std_logic_1164.all;

entity Dec4 is
    port(
        -- input
        Dec4_S: in std_logic_vector(1 downto 0);

        -- output
        Dec4_Out: out std_logic_vector(3 downto 0)
    );
end Dec4;

architecture logicFunction of Dec4 is
begin

    Dec4_Out(0) <= not Dec4_S(1) and not Dec4_S(0);
    Dec4_Out(1) <= not Dec4_S(1) and    Dec4_S(0);
    Dec4_Out(2) <=    Dec4_S(1) and not Dec4_S(0);
    Dec4_Out(3) <=    Dec4_S(1) and    Dec4_S(0);

end logicFunction;
```

A.8 Mux4

```
library ieee;
use ieee.std_logic_1164.all;

entity Mux4 is
    port(
        -- input
        Mux4_In: in std_logic_vector(3 downto 0);
        Mux4_S: in std_logic_vector(1 downto 0);

        -- output
        Mux4_Out: out std_logic
    );
end Mux4;

architecture logicFunction of Mux4 is
begin
    Mux4_Out <= (Mux4_In(0) and not Mux4_S(1) and not Mux4_S(0)) or
                (Mux4_In(1) and not Mux4_S(1) and Mux4_S(0)) OR
                (Mux4_In(2) and Mux4_S(1) and not Mux4_S(0)) OR
                (Mux4_In(3) and Mux4_S(1) and Mux4_S(0));
end logicFunction;
```

A.9 Counter4

```
library ieee;
use ieee.std_logic_1164.all;

entity Counter4 is
    port(

        -- input
        Counter4_CE: in std_logic;
        Counter4_CLK: in std_logic;
        Counter4_Reset: in std_logic;

        -- output
        Counter4_Q: out std_logic_vector(3 downto 0)

    );
end Counter4;

architecture logicFunction of Counter4 is

    component Adder4 is
        port(

            -- input
            Adder4_Ci: in std_logic;
            Adder4_A: in std_logic_vector(3 downto 0);
            Adder4_B: in std_logic_vector(3 downto 0);

            -- output
            Adder4_Co: out std_logic;
            Adder4_S: out std_logic_vector(3 downto 0)

        );
    end component;

    component Reg4 is
        port(

            -- input
            Reg4_In: in std_logic_vector(3 downto 0);
            Reg4_CE: in std_logic;
            Reg4_CLK: in std_logic;
            Reg4_Reset: in std_logic;

            -- output
            Reg4_Out: out std_logic_vector(3 downto 0)

        );
    end component;

    signal Q: std_logic_vector(3 downto 0);
    signal Adder4_S_to_Reg4_In: std_logic_vector(3 downto 0);

begin

    u0: Adder4 port map (
        Adder4_Ci => '0',
        Adder4_A => Q,
        Adder4_B => "0001",
        Adder4_S => Adder4_S_to_Reg4_In
    );
```

```
u1: Reg4 port map (  
    Reg4_In => Adder4_S_to_Reg4_In,  
    Reg4_CE => Counter4_CE,  
    Reg4_CLK => Counter4_CLK,  
    Reg4_Reset => Counter4_Reset,  
    Reg4_Out => Q  
);  
  
Counter4_Q <= Q;  
  
end logicFunction;
```

A.10 Adder4

```
library ieee;
use ieee.std_logic_1164.all;

entity Adder4 is
    port(

        -- input
        Adder4_Ci: in std_logic;
        Adder4_A: in std_logic_vector(3 downto 0);
        Adder4_B: in std_logic_vector(3 downto 0);

        -- output
        Adder4_Co: out std_logic;
        Adder4_S: out std_logic_vector(3 downto 0)

    );
end Adder4;

architecture logicFunction of Adder4 is

    component FullAdder is
        port(

            -- input
            FullAdder_A: in std_logic;
            FullAdder_B: in std_logic;
            FullAdder_Ci: in std_logic;

            -- output
            FullAdder_S: out std_logic;
            FullAdder_Co: out std_logic

        );
    end component;

    signal c0_to_c1: std_logic;
    signal c1_to_c2: std_logic;
    signal c2_to_c3: std_logic;

begin

    c0: FullAdder port map (
        FullAdder_A => Adder4_A(0),
        FullAdder_B => Adder4_B(0),
        FullAdder_Ci => Adder4_Ci,
        FullAdder_S => Adder4_S(0),
        FullAdder_Co => c0_to_c1
    );

    c1: FullAdder port map (
        FullAdder_A => Adder4_A(1),
        FullAdder_B => Adder4_B(1),
        FullAdder_Ci => c0_to_c1,
        FullAdder_S => Adder4_S(1),
        FullAdder_Co => c1_to_c2
    );

    c2: FullAdder port map (
        FullAdder_A => Adder4_A(2),
        FullAdder_B => Adder4_B(2),
        FullAdder_Ci => c1_to_c2,
```



```
FullAdder_S => Adder4_S(2),  
FullAdder_Co => c2_to_c3  
);  
  
c3: FullAdder port map (  
  FullAdder_A => Adder4_A(3),  
  FullAdder_B => Adder4_B(3),  
  FullAdder_Ci => c2_to_c3,  
  FullAdder_S => Adder4_S(3),  
  FullAdder_Co => Adder4_Co  
);  
  
end logicFunction;
```

A.11 Reg4

```
library ieee;
use ieee.std_logic_1164.all;

entity Reg4 is
  port(

    -- input
    Reg4_In: in std_logic_vector(3 downto 0);
    Reg4_CE: in std_logic;
    Reg4_CLK: in std_logic;
    Reg4_Reset: in std_logic;

    -- output
    Reg4_Out: out std_logic_vector(3 downto 0)

  );
end Reg4;

architecture logicFunction of Reg4 is
begin

  Reg4_Out(3) <= '0' when Reg4_Reset = '1' else Reg4_In(3) when rising_edge(Reg4_CLK) and Reg4_CE = '1';
  Reg4_Out(2) <= '0' when Reg4_Reset = '1' else Reg4_In(2) when rising_edge(Reg4_CLK) and Reg4_CE = '1';
  Reg4_Out(1) <= '0' when Reg4_Reset = '1' else Reg4_In(1) when rising_edge(Reg4_CLK) and Reg4_CE = '1';
  Reg4_Out(0) <= '0' when Reg4_Reset = '1' else Reg4_In(0) when rising_edge(Reg4_CLK) and Reg4_CE = '1';

end logicFunction;
```

A.12 FullAdder

```
library ieee;
use ieee.std_logic_1164.all;

entity FullAdder is
    port(

        -- input
        FullAdder_A: in std_logic;
        FullAdder_B: in std_logic;
        FullAdder_Ci: in std_logic;

        -- output
        FullAdder_S: out std_logic;
        FullAdder_Co: out std_logic

    );
end FullAdder;

architecture logicFunction of FullAdder is
begin

    FullAdder_S <= FullAdder_A xor FullAdder_B xor FullAdder_Ci;
    FullAdder_Co <= (FullAdder_A and FullAdder_B) or (FullAdder_Ci and (FullAdder_A xor FullAdder_B));

end logicFunction;
```

A.13 Ring Buffer

```
library ieee;
use ieee.std_logic_1164.all;

entity RingBuffer is
    port(

        -- input
        RingBuffer_D: in std_logic_vector(3 downto 0);
        RingBuffer_DAV: in std_logic;
        RingBuffer_CLK: in std_logic;
        RingBuffer_Reset: in std_logic;
        RingBuffer_CTS: in std_logic;

        -- output
        RingBuffer_Q: out std_logic_vector(3 downto 0);
        RingBuffer_Wreg: out std_logic;
        RingBuffer_DAC: out std_logic;

        debug_full: out std_logic;
        debug_empty: out std_logic

    );
end RingBuffer;

architecture logicFunction of RingBuffer is

    component RingBufferControl is
        port(

            -- input
            RingBufferControl_Reset: in std_logic;
            RingBufferControl_DAV: in std_logic;
            RingBufferControl_CTS: in std_logic;
            RingBufferControl_CLK: in std_logic;
            RingBufferControl_full: in std_logic;
            RingBufferControl_empty: in std_logic;

            -- output
            RingBufferControl_Wr: out std_logic;
            RingBufferControl_selPG: out std_logic;
            RingBufferControl_Wreg: out std_logic;
            RingBufferControl_DAC: out std_logic;
            RingBufferControl_incPut: out std_logic;
            RingBufferControl_incGet: out std_logic

        );
    end component;

    component MemoryAddressControl is
        port(

            -- input
            MemoryAddressControl_putget: in std_logic;
            MemoryAddressControl_CLK: in std_logic;
            MemoryAddressControl_incPut: in std_logic;
            MemoryAddressControl_incGet: in std_logic;
            MemoryAddressControl_Reset: in std_logic;

            -- output
            MemoryAddressControl_Address: out std_logic_vector(3 downto 0);
            MemoryAddressControl_full: out std_logic;
```

```

        MemoryAddressControl_empty: out std_logic

    );
end component;

component RAM is
    generic(
        ADDRESS_WIDTH : natural := 4;
        DATA_WIDTH : natural := 4
    );
    port(
        address : in std_logic_vector(ADDRESS_WIDTH - 1 downto 0);
        wr: in std_logic;
        din: in std_logic_vector(DATA_WIDTH - 1 downto 0);
        dout: out std_logic_vector(DATA_WIDTH - 1 downto 0)
    );
end component;

signal full: std_logic;
signal empty: std_logic;
signal Wr: std_logic;
signal selPG: std_logic;
signal incPut: std_logic;
signal incGet: std_logic;
SIGNAL Address: std_logic_vector(3 downto 0);

begin

u0: RingBufferControl port map (

    RingBufferControl_Reset => RingBuffer_Reset,
    RingBufferControl_DAV => RingBuffer_DAV,
    RingBufferControl_CTS => RingBuffer_CTS,
    RingBufferControl_CLK => RingBuffer_CLK,
    RingBufferControl_full => full,
    RingBufferControl_empty => empty,
    RingBufferControl_Wr => Wr,
    RingBufferControl_selPG => selPG,
    RingBufferControl_Wreg => RingBuffer_Wreg,
    RingBufferControl_DAC => RingBuffer_DAC,
    RingBufferControl_incPut => incPut,
    RingBufferControl_incGet => incGet

);

u1: MemoryAddressControl port map (

    MemoryAddressControl_putget => selPG,
    MemoryAddressControl_CLK => RingBuffer_CLK,
    MemoryAddressControl_incPut => incPut,
    MemoryAddressControl_incGet => incGet,
    MemoryAddressControl_Reset => RingBuffer_Reset,
    MemoryAddressControl_Address => Address,
    MemoryAddressControl_full => full,
    MemoryAddressControl_empty => empty

);

u2: RAM port map (

    address => Address,
    wr => Wr,

```

```
        din => RingBuffer_D,  
        dout => RingBuffer_Q  
  
    );  
  
    debug_full <= full;  
    debug_empty <= empty;  
  
end logicFunction;
```

A.14 Ring Buffer Control

```
library ieee;
use ieee.std_logic_1164.all;

entity RingBufferControl is
    port(

        -- input
        RingBufferControl_Reset: in std_logic;
        RingBufferControl_DAV: in std_logic;
        RingBufferControl_CTS: in std_logic;
        RingBufferControl_CLK: in std_logic;
        RingBufferControl_full: in std_logic;
        RingBufferControl_empty: in std_logic;

        -- output
        RingBufferControl_Wr: out std_logic;
        RingBufferControl_selPG: out std_logic;
        RingBufferControl_Wreg: out std_logic;
        RingBufferControl_DAC: out std_logic;
        RingBufferControl_incPut: out std_logic;
        RingBufferControl_incGet: out std_logic

    );
end RingBufferControl;

architecture logicFunction of RingBufferControl is

    type Tstate is (init, kd_addr, kd_write, kd_inc, kd_ack, ob_inc, ob_read);
    -- type Tstate is (start, writing, Wr_activate, incPut_activate, accepted_data, reading, incGet_activate);

    signal state: Tstate;
    signal next_state: Tstate;

begin

    state <= init when RingBufferControl_Reset = '1' else next_state when rising_edge(RingBufferControl_CLK);

    process(state, RingBufferControl_DAV, RingBufferControl_CTS, RingBufferControl_full, RingBufferControl_empty) begin
        case state is

            -- KD

            when init =>
                if RingBufferControl_DAV = '1' and RingBufferControl_full = '0' then
                    next_state <= kd_addr;
                elsif RingBufferControl_CTS = '1' and RingBufferControl_empty = '0' then
                    next_state <= ob_read;
                else
                    next_state <= init;
                end if;

            when kd_addr => next_state <= kd_write;
            when kd_write => next_state <= kd_inc;
            when kd_inc => next_state <= kd_ack;

            when kd_ack =>
                if RingBufferControl_DAV = '0' then
                    next_state <= init;
                else
                    next_state <= kd_ack;
                end if;

        end case;
    end process;
end logicFunction;
```

```
-- DB

when ob_read =>
    if RingBufferControl_CTS = '1' then
        next_state <= ob_read;
    else
        next_state <= ob_inc;
    end if;

when ob_inc => next_state <= init;

end case;
end process;

RingBufferControl_Wr <= '1' when state = kd_write else '0';
RingBufferControl_selPG <= '1' when state = kd_addr or state = kd_write else '0';
RingBufferControl_Wreg <= '1' when state = ob_read else '0';
RingBufferControl_DAC <= '1' when state = kd_ack else '0';
RingBufferControl_incPut <= '1' when state = kd_inc else '0';
RingBufferControl_incGet <= '1' when state = ob_inc else '0';

end logicFunction;
```


A.15 Memory Address Control

```
library ieee;
use ieee.std_logic_1164.all;

entity MemoryAddressControl is
    port(

        -- input
        MemoryAddressControl_putget: in std_logic;
        MemoryAddressControl_CLK: in std_logic;
        MemoryAddressControl_incPut: in std_logic;
        MemoryAddressControl_incGet: in std_logic;
        MemoryAddressControl_Reset: in std_logic;

        -- output
        MemoryAddressControl_Address: out std_logic_vector(3 downto 0);
        MemoryAddressControl_full: out std_logic;
        MemoryAddressControl_empty: out std_logic

    );
end MemoryAddressControl;

architecture logicFunction of MemoryAddressControl is

    component Counter4 is
        port(

            -- input
            Counter4_CE: in std_logic;
            Counter4_CLK: in std_logic;
            Counter4_Reset: in std_logic;

            -- output
            Counter4_Q: out std_logic_vector(3 downto 0)

        );
    end component;

    component CountUpDown is
        port(

            -- input
            CountUpDown_Up: in std_logic;
            CountUpDown_Down: in std_logic;
            CountUpDown_CLK: in std_logic;
            CountUpDown_Reset: in std_logic;

            -- output
            CountUpDown_Q: out std_logic_vector(4 downto 0)

        );
    end component;

    component Mux4_MAC is
        port(

            -- input
            Mux4_MAC_A: in std_logic_vector(3 downto 0);
            Mux4_MAC_B: in std_logic_vector(3 downto 0);
            Mux4_MAC_S: in std_logic;

            -- output
```

```

        Mux4_MAC_Out: out std_logic_vector(3 downto 0)

    );
end component;

signal incPut: std_logic;
signal incGet: std_logic;

signal get_addr: std_logic_vector(3 downto 0);
signal put_addr: std_logic_vector(3 downto 0);
signal size: std_logic_vector(4 downto 0);

signal full: std_logic;
signal empty: std_logic;

begin

    incPut <= '1' when MemoryAddressControl_incPut = '1' and full = '0' else '0';
    incGet <= '1' when MemoryAddressControl_incGet = '1' and empty = '0' else '0';

    u0: Counter4 port map (
        Counter4_CE => incGet,
        Counter4_CLK => MemoryAddressControl_CLK,
        Counter4_Reset => MemoryAddressControl_Reset,
        Counter4_Q => get_addr
    );

    u1: Counter4 port map (
        Counter4_CE => incPut,
        Counter4_CLK => MemoryAddressControl_CLK,
        Counter4_Reset => MemoryAddressControl_Reset,
        Counter4_Q => put_addr
    );

    u2: CountUpDown port map (
        CountUpDown_Up => incPut,
        CountUpDown_Down => incGet,
        CountUpDown_CLK => MemoryAddressControl_CLK,
        CountUpDown_Reset => MemoryAddressControl_Reset,
        CountUpDown_Q => size
    );

    u3: Mux4_MAC port map (
        Mux4_MAC_A => put_addr,
        Mux4_MAC_B => get_addr,
        Mux4_MAC_S => MemoryAddressControl_putget,
        Mux4_MAC_Out => MemoryAddressControl_Address
    );

    full <= '1' when size = "10000" else '0';
    MemoryAddressControl_full <= full;

    empty <= '1' when size = "00000" else '0';
    MemoryAddressControl_empty <= empty;

end logicFunction;

```

A.16 Mux4-MAC

```
library ieee;
use ieee.std_logic_1164.all;

entity Mux4_MAC is
    port(
        -- input
        Mux4_MAC_A: in std_logic_vector(3 downto 0);
        Mux4_MAC_B: in std_logic_vector(3 downto 0);
        Mux4_MAC_S: in std_logic;

        -- output
        Mux4_MAC_Out: out std_logic_vector(3 downto 0)
    );
end Mux4_MAC;

architecture logicFunction of Mux4_MAC is
begin
    Mux4_MAC_Out(0) <= (Mux4_MAC_A(0) and Mux4_MAC_S) or (Mux4_MAC_B(0) and not Mux4_MAC_S);
    Mux4_MAC_Out(1) <= (Mux4_MAC_A(1) and Mux4_MAC_S) or (Mux4_MAC_B(1) and not Mux4_MAC_S);
    Mux4_MAC_Out(2) <= (Mux4_MAC_A(2) and Mux4_MAC_S) or (Mux4_MAC_B(2) and not Mux4_MAC_S);
    Mux4_MAC_Out(3) <= (Mux4_MAC_A(3) and Mux4_MAC_S) or (Mux4_MAC_B(3) and not Mux4_MAC_S);
end logicFunction;
```

A.17 RAM

```
-----  
-- Project      : DE10-Lite  
-- Affiliations: DEETC, ISEL - IPL  
-- Funding      : -  
-----  
-- File         : RAM.vhd  
-- Author(s)    : Pedro Miguens Matutino  
-- Date         : 2023/01/03  
-----  
-- Copyright (c) 2023 Pedro Miguens Matutino  
-----  
-- Description :  
-- .  
-----  
  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
  
entity RAM is  
    generic(  
        ADDRESS_WIDTH : natural := 4;  
        DATA_WIDTH   : natural := 4  
    );  
    port(  
        address : in std_logic_vector(ADDRESS_WIDTH - 1 downto 0);  
        wr       : in std_logic;  
        din      : in std_logic_vector(DATA_WIDTH - 1 downto 0);  
        dout     : out std_logic_vector(DATA_WIDTH - 1 downto 0)  
    );  
end RAM;  
  
architecture behavioral of RAM is  
  
    type RAM_TYPE is array (0 to 2**ADDRESS_WIDTH - 1) of std_logic_vector(DATA_WIDTH - 1 downto 0);  
    signal ram : RAM_TYPE;  
  
begin  
  
    process(address, wr)  
    begin  
        dout <= ram(conv_integer(unsigned(address)));  
  
        if (wr='1') then  
            ram(conv_integer(unsigned(address))) <= din;  
        end if;  
    end process;  
  
end behavioral;
```

A.18 Output Buffer

```
library ieee;
use ieee.std_logic_1164.all;

entity OutputBuffer is
    port(

        -- input
        OutputBuffer_D: in std_logic_vector(3 downto 0);
        OutputBuffer_Load: in std_logic;
        OutputBuffer_ACK: in std_logic;
        OutputBuffer_Reset: in std_logic;
        OutputBuffer_CLK: in std_logic;

        -- output
        OutputBuffer_Q: out std_logic_vector(3 downto 0);
        OutputBuffer_OBfree: out std_logic;
        OutputBuffer_Dval: out std_logic

    );
end OutputBuffer;

architecture logicFunction of OutputBuffer is

    component BufferControl is
        port(

            -- input
            BufferControl_Reset: in std_logic;
            BufferControl_clk: in std_logic;
            BufferControl_Load: in std_logic;
            BufferControl_ACK: in std_logic;

            -- output
            BufferControl_OBfree: out std_logic;
            BufferControl_Wreg: out std_logic;
            BufferControl_Dval: out std_logic

        );
    end component;

    component Reg4 is
        port(

            -- input
            Reg4_In: in std_logic_vector(3 downto 0);
            Reg4_CE: in std_logic;
            Reg4_CLK: in std_logic;
            Reg4_Reset: in std_logic;

            -- output
            Reg4_Out: out std_logic_vector(3 downto 0)

        );
    end component;

    signal Wreg: std_logic;

begin

    u0: BufferControl port map (
        BufferControl_Reset => OutputBuffer_Reset,
```



ISEL

Departamento de Engenharia
Eletrónica e Telecomunicações
e de Computadores

Keyboard Decode (*Roulette Game*)

Laboratório de Informática e Computadores 2024 / 2025 verão

Autores: Ricardo Martins nº52326 / Bernardo Silva nº52605 / Bernardo Esteves nº52948

```
        BufferControl_clk => OutputBuffer_CLK,
        BufferControl_Load => OutputBuffer_Load,
    BufferControl_ACK => OutputBuffer_ACK,
        BufferControl_OBfree => OutputBuffer_OBfree,
        BufferControl_Wreg => Wreg,
    BufferControl_Dval => OutputBuffer_Dval
);

u1: Reg4 port map (
    Reg4_In => OutputBuffer_D,
    Reg4_CE => '1',
    Reg4_CLK => Wreg,
    Reg4_Reset => OutputBuffer_Reset,
    Reg4_Out => OutputBuffer_Q
);

end logicFunction;
```

A.19 BufferControl

```
library ieee;
use ieee.std_logic_1164.all;

entity BufferControl is
    port(

        -- input
        BufferControl_Reset: in std_logic;
        BufferControl_clk: in std_logic;
        BufferControl_Load: in std_logic;
        BufferControl_ACK: in std_logic;

        -- output
        BufferControl_OBfree: out std_logic;
        BufferControl_Wreg: out std_logic;
        BufferControl_Dval: out std_logic

    );
end BufferControl;

architecture logicFunction of BufferControl is

    type Tstate is (start, data_available, ack_received);

    signal state: Tstate := start;
    signal next_state: Tstate := start;

begin

    state <= start when BufferControl_Reset = '1' else next_state when rising_edge(BufferControl_clk);

    process(state, BufferControl_Load, BufferControl_ACK) begin

        case state is

            when start =>
                if BufferControl_Load = '1' then
                    next_state <= data_available;
                else
                    next_state <= start;
                end if;

            when data_available =>
                if BufferControl_ACK = '1' then
                    next_state <= ack_received;
                else
                    next_state <= data_available;
                end if;

            when ack_received =>
                if BufferControl_ACK = '1' then
                    next_state <= ack_received;
                else
                    next_state <= start;
                end if;

        end case;

    end process;

    BufferControl_Wreg <= '1' when (state = start and BufferControl_Load = '1') else '0';
    BufferControl_OBfree <= '1' when (state = start) else '0';
```

```
BufferControl_Dval <= '1' when (state = data_available) else '0';  
  
end logicFunction;
```


B *Kotlin*

B.1 HAL

Algoritmo 1: HAL - Hardware Abstract Layer

```
import isel.leic.UsbPort

object HAL {

    /** ltimo _output_ enviado. */
    var lastOutput = 0

    /** Inicializa o _output_ do UsbPort. */
    fun init() = UsbPort.write(0)

    /** Verifica se os bits da `mask` est o ativos no _input_ do UsbPort. */
    fun isBit(mask: Int) = readBits(mask) == mask

    /** Retorna os bits no _input_ do UsbPort filtrados por `mask`. */
    fun readBits(mask: Int) = UsbPort.read() and mask

    /** Escreve no _output_ do UsbPort `value` filtrado por `mask`. */
    fun writeBits(mask: Int, value: Int) = write((value and mask) or (lastOutput and mask.inv()))

    /** Ativa no _output_ do UsbPort os bits da `mask`. */
    fun setBits(mask: Int) = write(lastOutput or mask)

    /** Desativa no _output_ do UsbPort os bits da `mask`. */
    fun clearBits(mask: Int) = write(lastOutput and mask.inv())

    /** Escreve no _output_ do UsbPort e guarda o que escreveu. */
    private fun write(output: Int){
        UsbPort.write(output)
        lastOutput = output
    }

}

fun main(){
    HAL.init()

    while(true){
        println(HAL.readBits(0xF).toString(2))
        readln()
    }
}
```

B.2 KBD

Algoritmo 2: KBD

```
import isel.leic.utils.Time

// Ler teclas. Fun es retornam '0'..'9', 'A'..'D', '#', '*' ou NONE
object KBD {

    private const val NONE = 0.toChar()

    private const val KEYPAD = "147*2580369#ABCD"

    private const val KEY_MASK = 0b00001111 // input
    private const val VAL_MASK = 0b00010000 // input

    private const val ACK_MASK = 0b10000000 // output

    /** Inicializa o teclado. */
    fun init(){

        // Garantir que nenhuma tecla acknowledged no nicio
        HAL.clearBits(ACK_MASK)

    }

    /** Retorna de imediato a tecla premida ou `NONE` se n o h tecla premida. */
    fun getKey(): Char {

        // Verificar se existe alguma tecla premida
        if (!HAL.isBit(VAL_MASK)) return NONE

        // Receber tecla premida
        val i = HAL.readBits(KEY_MASK)
        check(i in 0 until KEYPAD.length) { "Invalid key code (0x${Integer.toHexString(i)})" }

        // Acknowledge
        HAL.setBits(ACK_MASK)
        while (HAL.isBit(VAL_MASK)) {} // Esperar que acknowledge seja recebido
        HAL.clearBits(ACK_MASK)

        return KEYPAD[i]
    }

    /**
     * Retorna a tecla premida ou `NONE` caso o `timeout` passe.
     * @property timeout Milissegundos at deixar de esperar.
     */
    fun waitKey(timeout: Long): Char {

        val end = Time.getTimeInMillis() + timeout

        while (Time.getTimeInMillis() < end){
            val key = getKey()
            if (key != NONE) return key
        }

        return NONE
    }
}

fun main(){
    KBD.init()
    // println("start")
    // Time.sleep(10000)
    // println("print")
    while(true)
        print(KBD.waitKey(60_000L))
}
```

B.3 TUI

Algoritmo 3: KBD

```
import isel.leic.utils.Time
import util.Alignment

object TUI {

  /** 9+ - Para indicar que h mais de 9 cr ditos */
  const val NINE_PLUS = 0.toChar()

  /** Emoticon feliz - Para vit rias */
  const val HAPPY = 1.toChar()

  /** Emoticon triste - Para perdas */
  const val SAD = 2.toChar()

  /** S mbolo de Manuten o */
  const val MAINTENANCE = 3.toChar()

  /** Seta para a direita */
  const val ARROW = 4.toChar()

  /** Inicializa o TUI. */
  fun init(){

    LCD.clear()

    LCD.loadChar(NINE_PLUS, listOf(
      "###_ _",
      "#_ _ _",
      "###_ _",
      "_ _ _ _",
      "###_ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _"
    ))

    LCD.loadChar(HAPPY, listOf(
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _"
    ))

    LCD.loadChar(SAD, listOf(
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _"
    ))

    LCD.loadChar(MAINTENANCE, listOf(
      "####",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      "####"
    ))
  }
}
```

```

LCD.loadChar(ARROW, listOf(
    "UUUUU",
    "UU#UU",
    "UUU#U",
    "####",
    "UUU#U",
    "UU#UU",
    "UUUUU",
    "UUUUU"
))

}

/* ----- LCD ----- */

/**
 * Escreve texto.
 * @property align Alinhamento.
 * @property range Limites do texto.
 */
fun write(text: String, line: Int, align: Alignment = Alignment.CENTER, range: IntRange = 0..LCD.COLS){
    require(line in 0 until LCD.LINES) { "Invalid_line." }

    val rangeSize = range.last - range.start
    val startCol = range.start + when(align){
        Alignment.LEFT -> 0
        Alignment.CENTER -> (rangeSize - text.length) / 2
        Alignment.RIGHT -> rangeSize - text.length
    }

    updateLine(line, text, startCol)
}

/**
 * Atualiza a frame de anima o de um texto rotativo.
 *
 * til para mostrar texto maior do que a largura do LCD.
 */
fun scrollText(text: String, line: Int, speed: Int = 250, range: IntRange = 0..LCD.COLS){
    require(line in 0 until LCD.LINES) { "Invalid_line." }

    val time = Time.getTimeInMillis() / speed
    val rangeSize = range.last - range.start

    val text = "$text_" // Adicionar espaço como margem
    var res = text.substring((time % text.length).toInt()) // Cortar texto
    while(res.length < rangeSize) res += text // Duplicar texto para ocupar espaço inteiro
    res = res.substring(0 until rangeSize) // Manter texto dentro do range

    updateLine(line, res, range.start)
}

fun clear(){
    line0 = List(LCD.COLS){ " " }.joinToString("")
    line1 = List(LCD.COLS){ " " }.joinToString("")
    LCD.clear()
}

private var line0 = List(LCD.COLS){ " " }.joinToString("")
private var line1 = List(LCD.COLS){ " " }.joinToString("")

/** Atualiza as linhas do LCD evitando comandos redundantes. */
private fun updateLine(line: Int, text: String, start: Int = 0){
    // Obter último estado da linha
    val lastLine = when(line){
        0 -> line0
        1 -> line1
        else -> throw IllegalArgumentException("Invalid_line.")
    }

    // Sobrescrever linha

```

```

val prefix = if(start > 0) lastLine.substring(0 until start) else ""
val suffix = if(start + text.length <= LCD.COLS) lastLine.substring(start + text.length) else ""
val currLine = (prefix + text + suffix).substring(0 until LCD.COLS)

// Ignorar se n o existir altera es
if(lastLine == currLine) return

// Escrever caract res nos locais necess rios
var col: Int? = null
repeat(LCD.COLS){ i ->
    if(lastLine[i] == currLine[i]) return@repeat

    if(col != i) LCD.cursor(line , i)
    LCD.write(currLine[i])
    col = (col ?: 0) + 1
}

// Atualizar ltime estado da linha
when(line){
    0 -> line0 = currLine
    1 -> line1 = currLine
}

}

/* ----- Keyboard ----- */

/** Retorna de imediato a tecla premida ou `NONE` se n o h tecla premida. */
fun getKey() = KBD.getKey()

}

fun main(){
    HAL.init()
    SerialEmitter.init()
    LCD.init()
    TUI.init()

    while(true){
        TUI.scrollText("If you are seeing this text scrolling , it means that the TUI is working!", 0)

        val key = TUI.getKey()
        if(key != 0.toChar()) TUI.write(key.toString(), 1)
    }
}

```