

1 SLCDC

O bloco SLCDC faz a ligação do módulo *Control* com o LCD no qual, recebe em série 5 bits de informação e 1 bit de paridade. Dentro destes 5 bits o 1 é o bit RS no qual, indica se a mensagem é de controlo ou de dados, os próximos 4 bits entregam os dados necessários ao LCD e o último bit contém a paridade ímpar. A implementação do SLCDC foi fundamentada através da Figura 1 no qual, é possível ver o diagrama de blocos resultante da nossa implementação na Figura 2.

 


Figura 1: Diagrama de Blocos do *SLCDC*

 


Figura 2: Diagrama de Blocos do módulo *SLCDC*

2 Serial Receiver

O *Serial Receiver* tem como função tratar do recebimento dos dados vindo do *Control*, detetando o bit de paridade para confirmar que não houve erros de transmissão, separar quando são os bits de dados ou de paridade e por fim enviar para o *LCD Dispatcher*. Assim sendo, o *Serial Receiver* contém 4 componentes sendo eles o *Serial Control*, *Parity Check*, *Shift Register* e *Counter*. É também feito no *Serial Receiver* a ligação das flags pFlag e dFlag que quando o *Counter* contar até 5 bits irá ligar a dFlag correspondente aos dados e quando contar até 6 bits irá ligar a pFlag correspondente à paridade. Os números no bloco *SRC* irão ser diferentes devido ao invés de receber 5 bits recebe 8. Como base para a conceção do mesmo foi usado o diagrama de blocos correspondente à figura 3. O diagrama de blocos que representa o *Serial Receiver* está representado na 4.

 


Figura 3: Diagrama de Blocos do *Serial Receiver*

 


Figura 4: Diagrama de Blocos do módulo *Serial Receiver*

2.1 Serial Control

O *Serial Control* faz o controlo dos dados recebidos pelo *Control*, manuseando assim quando os outros componentes do *Serial Receiver* devem ou não ser ligados e transmitindo se os dados são válidos ou não. O ASM-Chart produzido ao implementar o *Serial Control* está representado na Figura 5 e o diagrama de blocos correspondente na Figura 6.

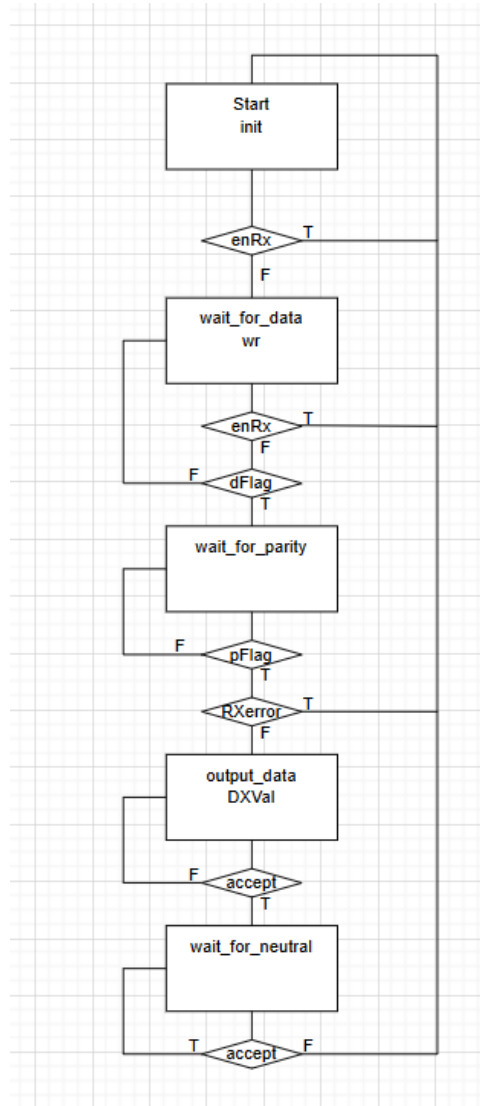


Figura 5: ASM Chart do *Serial Control*



Figura 6: Diagrama de Blocos do módulo *Serial Control*

2.2 Parity Check

Parity Check é o componente responsável por validar a paridade ímpar no qual é iniciado pelo *Serial Control* e a sua saída será 0 quando o número de 1's for ímpar e será 1 quando o número de 1's for par. Assim o resultado da nossa implementação está disponível no diagrama de blocos da Figura 7.

 


Figura 7: Diagrama de Blocos do módulo *Parity Check*

2.3 Shift Register

O bloco *Shift Register* também é ligado pelo *Serial Control* e tem como função enviar cada bit individualmente para o *LCD Dispatcher* transmitindo assim apenas os bits de dados. Com isto, o diagrama de blocos correspondente ao *Shift Register* está representado na Figura 8.

 


Figura 8: Diagrama de Blocos do módulo *Shift Register*

2.4 Counter

O componente *Counter* ao ser ativado pelo *Serial Control* tem a função de contar quantos bits são recebidos pelo *Serial Receiver* assim, o diagrama de bloco do *Counter* está demonstrado na Figura 9.

 


Figura 9: Diagrama de Blocos do módulo *Counter*

3 LCD Dispatcher

Por fim, temos o bloco *LCD Dispatcher* que é responsável por entregar as dados válidas do *Serial Receiver* ao *LCD* enviando assim, os bits de dados, RS e de paridade e o sinal Wrl para posteriormente ligar o LCD. Para a conceção do *LCD Dispatcher* foi preciso conceber uma máquina de estados podendo ser visualizada na 10. O ASM-Chart ficou com 12 estados de esperar devido ao clock ser 20 ns e o tempo necessário para os dados serem enviados para o LCD serem 236ns. O diagrama de blocos condizente com o *LCD Dispatcher* está representado na Figura 11.

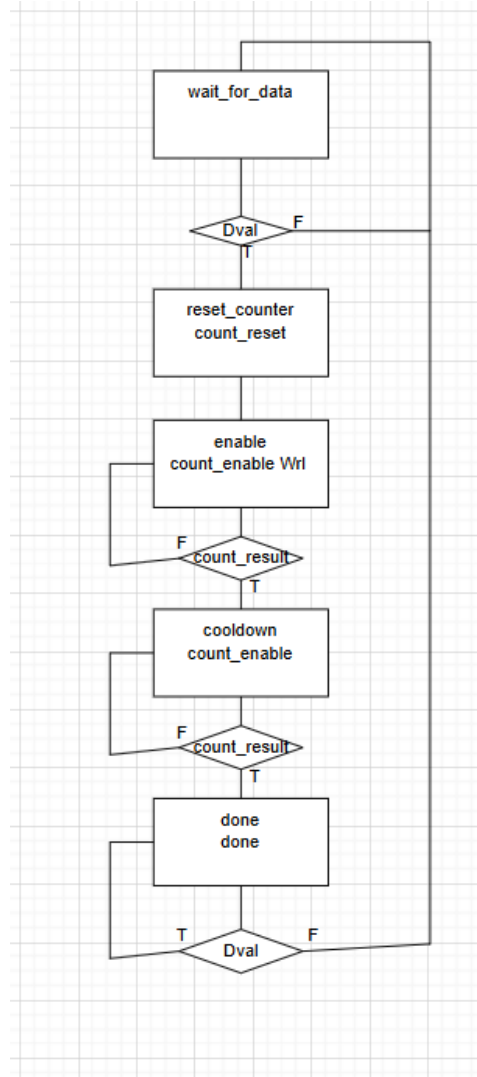


Figura 10: ASM-Chart do *LCD Dispatcher*

 


Figura 11: Diagrama de Blocos do módulo *LCD Dispatcher*

4 Conclusões

Em conclusão, o desenvolvimento do SLCDC apresentou sérias dificuldades e complexidades durante todo o seu desenvolvimento desde o ASM-Chart do bloco *Serial Control*, a implementação do *Parity Check* com a paridade ímpar e principalmente a conceção do *LCD Dispatcher* pois, o tempo necessário para transmitir os dados para o LCD causou sérios desafios e problemas.

A VHDL

A.1 Roleta

```
library ieee;
use ieee.std_logic_1164.all;

entity Roleta is
    port(

        -- input
        CLK: in std_logic;
        Reset: in std_logic;
        KBD_KeyLin: in std_logic_vector(3 downto 0);
        Coin: in std_logic;
        CoinID: in std_logic;
        Maintenance_in: in std_logic;

        -- output
        KBD_KeyCol: out std_logic_vector(3 downto 0);
        LCD_E: out std_logic;
        LCD_RS: out std_logic;
        LCD_D: out std_logic_vector(7 downto 0);
        RD_HEX0: out std_logic_vector(7 downto 0);
        RD_HEX1: out std_logic_vector(7 downto 0);
        RD_HEX2: out std_logic_vector(7 downto 0);
        RD_HEX3: out std_logic_vector(7 downto 0);
        RD_HEX4: out std_logic_vector(7 downto 0);
        RD_HEX5: out std_logic_vector(7 downto 0);
        Accept: out std_logic;

        debug_full: out std_logic;
        debug_empty: out std_logic

    );
end Roleta;

architecture logicFunction of Roleta is

    component UsbPort is
        port(

            -- input
            inputPort: in std_logic_vector(7 downto 0);

            -- output
            outputPort: out std_logic_vector(7 DOWNT0 0)

        );
    end component;

    component KeyboardReader is
        port(

            -- input
            KeyboardReader_Ack: in std_logic;
            KeyboardReader_Lin: in std_logic_vector(3 downto 0);
            KeyboardReader_CLK: in std_logic;
            KeyboardReader_Reset: in std_logic;

            -- output
            KeyboardReader_Col: out std_logic_vector(3 downto 0);
```




```
KeyboardReader_Dval: out std_logic;
KeyboardReader_Q: out std_logic_vector(3 downto 0);

debug_full: out std_logic;
debug_empty: out std_logic

);
end component;

component SLCDC is
port(

    -- input
    SLCDC_Reset: in std_logic;
    SLCDC_LCDSel: in std_logic;
    SLCDC_SCLK: in std_logic;
    SLCDC_CLK: in std_logic;
    SLCDC_SDx: in std_logic;

    -- output
    SLCDC_E: out std_logic;
    SLCDC_D: out std_logic_vector(4 downto 0)

);
end component;

component SRC is
port(

    -- input
    SRC_Reset: in std_logic;
    SRC_RDSel: in std_logic;
    SRC_SCLK: in std_logic;
    SRC_CLK: in std_logic;
    SRC_SDx: in std_logic;

    -- output
    SRC_set: out std_logic;
    SRC_D: out std_logic_vector(7 downto 0)

);
end component;

component rouletteDisplay is
port(

    -- input
    set: in std_logic;
    cmd: in std_logic_vector(2 downto 0);
    data: in std_logic_vector(4 downto 0);

    -- output
    HEX0: out std_logic_vector(7 downto 0);
    HEX1: out std_logic_vector(7 downto 0);
    HEX2: out std_logic_vector(7 downto 0);
    HEX3: out std_logic_vector(7 downto 0);
    HEX4: out std_logic_vector(7 downto 0);
    HEX5: out std_logic_vector(7 downto 0)

);
end component;

component CoinAcceptor is
```

```

port(

    -- input
    CoinAcceptor_Accept_in: in std_logic;
    CoinAcceptor_Coin_in: in std_logic;
    CoinAcceptor_CoinID_in: in std_logic;

    -- output
    CoinAcceptor_Accept_out: out std_logic;
    CoinAcceptor_Coin_out: out std_logic;
    CoinAcceptor_CoinID_out: out std_logic

);
end component;

component Maintenance is
port(

    -- input
    Maintenance_in: in std_logic;

    -- output
    Maintenance_out: out std_logic

);
end component;

-- Input (Hardware → Software)
signal usb_input: std_logic_vector(7 downto 0);

-- Output (Software → Hardware)
signal usb_output: std_logic_vector(7 downto 0);

signal RD_set: std_logic;
signal RD_cmd: std_logic_vector(2 downto 0);
signal RD_data: std_logic_vector(4 downto 0);

-- signal tmp: std_logic_vector(9 downto 0);

begin

u0: UsbPort port map (
    inputPort => usb_input,
    outputPort => usb_output
);

u1: KeyboardReader port map (
    KeyboardReader_Ack => usb_output(7),
    KeyboardReader_Lin => KBD_KeyLin,
    KeyboardReader_CLK => CLK,
    KeyboardReader_Reset => Reset,
    KeyboardReader_Col => KBD_KeyCol,
    KeyboardReader_Dval => usb_input(4),
    KeyboardReader_Q => usb_input(3 downto 0),
    debug_empty => debug_empty,
    debug_full => debug_full
);

u2: SLCDC port map (
    SLCDC_Reset => Reset,
    SLCDC_LCDSel => usb_output(0),

```

```
SLCDC_SCLK => usb_output(4),
SLCDC_CLK => CLK,
SLCDC_SDx => usb_output(3),
SLCDC_E => LCD_E,
SLCDC_D(0) => LCD_RS,
SLCDC_D(4 downto 1) => LCD_D(7 downto 4)
);

u3: SRC port map (
  SRC_Reset => Reset,
  SRC_RDsel => usb_output(1),
  SRC_SCLK => usb_output(4),
  SRC_CLK => CLK,
  SRC_SDx => usb_output(3),
  SRC_set => RD_set,
  SRC_D(2 downto 0) => RD_cmd,
  SRC_D(7 downto 3) => RD_data
);

u4: rouletteDisplay port map (
  set => RD_set,
  cmd => RD_cmd,
  data => RD_data,
  HEX0 => RD_HEX0,
  HEX1 => RD_HEX1,
  HEX2 => RD_HEX2,
  HEX3 => RD_HEX3,
  HEX4 => RD_HEX4,
  HEX5 => RD_HEX5
);

u5: CoinAcceptor port map (
  CoinAcceptor_Accept_in => usb_output(6),
  CoinAcceptor_Coin_in => Coin,
  CoinAcceptor_CoinID_in => CoinID,
  CoinAcceptor_Accept_out => Accept,
  CoinAcceptor_Coin_out => usb_input(6),
  CoinAcceptor_CoinID_out => usb_input(5)
);

u6: Maintenance port map (
  Maintenance_in => Maintenance_in,
  Maintenance_out => usb_input(7)
);

end logicFunction;
```

A.2 UsbPort

```
-- Copyright (C) 2020 Intel Corporation. All rights reserved.
-- Your use of Intel Corporation's design tools, logic functions
-- and other software and tools, and any partner logic
-- functions, and any output files from any of the foregoing
-- (including device programming or simulation files), and any
-- associated documentation or information are expressly subject
-- to the terms and conditions of the Intel Program License
-- Subscription Agreement, the Intel Quartus Prime License Agreement,
-- the Intel FPGA IP License Agreement, or other applicable license
-- agreement, including, without limitation, that your use is for
-- the sole purpose of programming logic devices manufactured by
-- Intel and sold by Intel or its authorized distributors. Please
-- refer to the applicable agreement for further details, at
-- https://fpgasoftware.intel.com/eula.

-- PROGRAM          "Quartus Prime"
-- VERSION          "Version 20.1.1 Build 720 11/11/2020 SJ Lite Edition"
-- CREATED          "Tue Mar 01 09:42:31 2022"

library ieee;
use ieee.std_logic_1164.all;

library work;

entity UsbPort is
    port(
        inputPort: in std_logic_vector(7 downto 0);
        outputPort: out std_logic_vector(7 downto 0)
    );
end UsbPort;

architecture bdf_type of UsbPort is

    component sld_virtual_jtag
        GENERIC(
            lpm_type: string;
            sld_auto_instance_index: string;
            sld_instance_index: integer;
            sld_ir_width: integer;
            sld_sim_action: string;
            sld_sim_n_scan: integer;
            sld_sim_total_length: integer
        );
    PORT(
        tdo: in std_logic;
        ir_out: in std_logic_vector(7 downto 0);
        tck: out std_logic;
        tdi: out std_logic;
        virtual_state_cdr: out std_logic;
        virtual_state_sdr: out std_logic;
        virtual_state_e1dr: out std_logic;
        virtual_state_pdr: out std_logic;
        virtual_state_e2dr: out std_logic;
        virtual_state_uds: out std_logic;
        virtual_state_cir: out std_logic;
        virtual_state_uir: out std_logic;
        tms: out std_logic;
        jtag_state_tlr: out std_logic;
        jtag_state_rti: out std_logic;
        jtag_state_sdrs: out std_logic;
        jtag_state_cdr: out std_logic;
```



```
jtag_state_sdr: out std_logic;
jtag_state_e1dr: out std_logic;
jtag_state_pdr: out std_logic;
jtag_state_e2dr: out std_logic;
jtag_state_udr: out std_logic;
jtag_state_sirs: out std_logic;
jtag_state_cir: out std_logic;
jtag_state_sir: out std_logic;
jtag_state_e1ir: out std_logic;
jtag_state_pir: out std_logic;
jtag_state_e2ir: out std_logic;
jtag_state_uir: out std_logic;
ir_in: out std_logic_vector(7 downto 0)
);
end component;

begin

b2v_inst: sld_virtual_jtag
  generic map (
    lpm_type => "sld_virtual_jtag",
    sld_auto_instance_index => "YES",
    sld_instance_index => 0,
    sld_ir_width => 8,
    sld_sim_action => "UNUSED",
    sld_sim_n_scan => 0,
    sld_sim_total_length => 0
  )
  port map (
    ir_out => inputPort,
    ir_in => outputPort
  );

end bdf_type;
```

A.3 SLCDC

```
library ieee;
use ieee.std_logic_1164.all;

entity SLCDC is
    port(

        -- input
        SLCDC_Reset: in std_logic;
        SLCDC_LCDSel: in std_logic;
        SLCDC_SCLK: in std_logic;
        SLCDC_CLK: in std_logic;
        SLCDC_SDx: in std_logic;

        -- output
        SLCDC_E: out std_logic;
        SLCDC_D: out std_logic_vector(4 downto 0)
    );
end SLCDC;

architecture logicFunction of SLCDC is

    component LCDSerialReceiver is
        port(

            -- input
            LCDSerialReceiver_Reset: in std_logic;
            LCDSerialReceiver_SS: in std_logic;
            LCDSerialReceiver_SCLK: in std_logic;
            LCDSerialReceiver_CLK: in std_logic;
            LCDSerialReceiver_SDx: in std_logic;
            LCDSerialReceiver_accept: in std_logic;

            -- output
            LCDSerialReceiver_DXval: out std_logic;
            LCDSerialReceiver_D: out std_logic_vector(4 downto 0)
        );
    end component;

    component LCDDispatcher is
        port(

            -- input
            LCDDispatcher_Reset: in std_logic;
            LCDDispatcher_Dval: in std_logic;
            LCDDispatcher_Din: in std_logic_vector(4 downto 0);
            LCDDispatcher_CLK: in std_logic;

            -- output
            LCDDispatcher_Wrl: out std_logic;
            LCDDispatcher_Dout: out std_logic_vector(4 downto 0);
            LCDDispatcher_done: out std_logic
        );
    end component;

    signal val: std_logic;
    signal D: std_logic_vector(4 downto 0);
    signal done_to_accept: std_logic;

begin
```

```
u0: LCDSerialReceiver port map (  
    LCDSerialReceiver_Reset => SLCDC_Reset,  
    LCDSerialReceiver_SS => SLCDC_LCDSel,  
    LCDSerialReceiver_SCLK => SLCDC_SCLK,  
    LCDSerialReceiver_CLK => SLCDC_CLK,  
    LCDSerialReceiver_SDx => SLCDC_SDx,  
    LCDSerialReceiver_accept => done_to_accept,  
    LCDSerialReceiver_Dxval => val,  
    LCDSerialReceiver_D => D  
);  
  
u1: LCDDispatcher port map (  
    LCDDispatcher_Reset => SLCDC_Reset,  
    LCDDispatcher_Dval => val,  
    LCDDispatcher_Din => D,  
    LCDDispatcher_CLK => SLCDC_CLK,  
    LCDDispatcher_Wrl => SLCDC_E,  
    LCDDispatcher_Dout => SLCDC_D,  
    LCDDispatcher_done => done_to_accept  
);  
  
end logicFunction;
```

A.4 LCDSerialReceiver

```
library ieee;
use ieee.std_logic_1164.all;

entity LCDSerialReceiver is
    port(

        -- input
        LCDSerialReceiver_SS: in std_logic;
        LCDSerialReceiver_SCLK: in std_logic;
        LCDSerialReceiver_CLK: in std_logic;
        LCDSerialReceiver_Reset: in std_logic;
        LCDSerialReceiver_SDX: in std_logic;
        LCDSerialReceiver_accept: in std_logic;

        -- output
        LCDSerialReceiver_DXval: out std_logic;
        LCDSerialReceiver_D: out std_logic_vector(4 downto 0)
    );
end LCDSerialReceiver;

architecture logicFunction of LCDSerialReceiver is

    component SerialControl is port (

        -- input
        SerialControl_Reset: in std_logic;
        SerialControl_enRX: in std_logic;
        SerialControl_accept: in std_logic;
        SerialControl_pFlag: in std_logic;
        SerialControl_dFlag: in std_logic;
        SerialControl_RXerror: in std_logic;
        SerialControl_Clk: in std_logic;

        -- output
        SerialControl_wr: out std_logic;
        SerialControl_init: out std_logic;
        SerialControl_DXval: out std_logic

    );
end component;

    component ShiftRegister5 is
        port(

            -- input
            ShiftRegister5_data: in std_logic;
            ShiftRegister5_clk: in std_logic;
            ShiftRegister5_enableShift: in std_logic;
            ShiftRegister5_Reset: in std_logic;

            -- output
            ShiftRegister5_D: out std_logic_vector(4 downto 0)

        );
    end component;

    component ParityCheck is
        port(

            -- input
            ParityCheck_data: in std_logic;
```



```

        ParityCheck_init: in std_logic;
        ParityCheck_clk: in std_logic;

        -- output
        ParityCheck_err: out std_logic

    );
end component;

component Counter3 is
    port(

        -- input
        Counter3_CE: in std_logic;
        Counter3_CLK: in std_logic;
        Counter3_Reset: in std_logic;

        -- output
        Counter3_Q: out std_logic_vector(2 downto 0)

    );
end component;

signal pFlag: std_logic;
signal dFlag: std_logic;
signal error: std_logic;
signal RXerror: std_logic;
signal wr: std_logic;
signal init: std_logic;
signal counter: std_logic_vector(2 downto 0);

begin

    u0: SerialControl port map (
        SerialControl_Reset => LCDSerialReceiver_Reset,
        SerialControl_enRX => LCDSerialReceiver_SS,
        SerialControl_accept => LCDSerialReceiver_Accept,
        SerialControl_pFlag => pFlag,
        SerialControl_dFlag => dFlag,
        SerialControl_RXerror => RXerror,
        SerialControl_Clk => LCDSerialReceiver_CLK,
        SerialControl_wr => wr,
        SerialControl_init => init,
        SerialControl_DXval => LCDSerialReceiver_DXval
    );

    RXerror <= error and not LCDSerialReceiver_SCLK;

    u1: ShiftRegister5 port map (
        ShiftRegister5_data => LCDSerialReceiver_SDX,
        ShiftRegister5_clk => LCDSerialReceiver_SCLK,
        ShiftRegister5_Reset => LCDSerialReceiver_Reset,
        ShiftRegister5_enableShift => wr,
        ShiftRegister5_D => LCDSerialReceiver_D
    );

    u2: ParityCheck port map (
        ParityCheck_data => LCDSerialReceiver_SDX,
        ParityCheck_init => init,
        ParityCheck_clk => LCDSerialReceiver_SCLK,
        ParityCheck_err => error
    );

```

```
u3: Counter3 port map (  
    Counter3_CE => '1',  
    Counter3_CLK => LCDSerialReceiver_SCLK,  
    Counter3_Reset => init,  
    Counter3_Q => counter  
);  
  
dFlag <= counter(2) and not counter(1) and counter(0) and not LCDSerialReceiver_SCLK;  
pflag <= counter(2) and counter(1) and not counter(0) and not LCDSerialReceiver_SCLK;  
  
end logicFunction;
```

A.5 SerialControl

```
library ieee;
use ieee.std_logic_1164.all;

entity SerialControl is
    port(

        -- input
        SerialControl_Reset: in std_logic;
        SerialControl_enRX: in std_logic;
        SerialControl_accept: in std_logic;
        SerialControl_pFlag: in std_logic;
        SerialControl_dFlag: in std_logic;
        SerialControl_RXerror: in std_logic;
        SerialControl_Clk: in std_logic;

        -- output
        SerialControl_wr: out std_logic;
        SerialControl_init: out std_logic;
        SerialControl_DXval: out std_logic

    );
end SerialControl;

architecture logicFunction of SerialControl is

    type Tstate is (start, wait_for_data, wait_for_parity, output_data, wait_for_neutral);

    signal state: Tstate;
    signal next_state: Tstate;

begin

    state <= start when SerialControl_Reset = '1' else next_state when rising_edge(SerialControl_Clk);

    process(state, SerialControl_enRX, SerialControl_accept, SerialControl_pFlag, SerialControl_dFlag, SerialControl_RXerror)

        case state is

            when start =>
                if SerialControl_enRX = '0' then
                    next_state <= wait_for_data;
                else
                    next_state <= start;
                end if;

            when wait_for_data =>
                if SerialControl_enRX = '0' then
                    if SerialControl_dFlag = '1' then
                        next_state <= wait_for_parity;
                    else
                        next_state <= wait_for_data;
                    end if;
                else
                    next_state <= start;
                end if;

            when wait_for_parity =>
                --if SerialControl_enRX = '1' then
                if SerialControl_pFlag = '1' then
                    if SerialControl_RXerror = '0' then
                        next_state <= output_data;
                    end if;
                end if;
            end case;

        end process;
    end architecture;
```



ISEL

Departamento de Engenharia
Eletrónica e Telecomunicações
e de Computadores

SLCDC (*Roulette Game*)

Laboratório de Informática e Computadores 2024 / 2025 verão

Autores: Ricardo Martins nº52326 / Bernardo Silva nº52605 / Bernardo Esteves nº52948

```
        else
            next_state <= start;
        end if;
    else
        next_state <= wait_for_parity;
    end if;
--else
    --next_state <= wait_for_parity;
--end if;

when output_data =>
    if SerialControl_accept = '1' then
        next_state <= wait_for_neutral;
    else
        next_state <= output_data;
    end if;

    when wait_for_neutral =>
        if SerialControl_accept = '0' then
            next_state <= start;
        else
            next_state <= wait_for_neutral;
        end if;

    end case;
end process;

SerialControl_DXval <= '1' when (state = output_data) else '0';
SerialControl_wr <= '1' when (state = wait_for_data) else '0';
SerialControl_init <= '1' when (state = start) else '0';

end logicFunction;
```

A.6 ParityCheck

```
library ieee;
use ieee.std_logic_1164.all;

entity ParityCheck is
    port(
        -- input
        ParityCheck_data: in std_logic;
        ParityCheck_init: in std_logic;
        ParityCheck_clk: in std_logic;

        -- output
        ParityCheck_err: out std_logic
    );
end ParityCheck;

architecture logicFunction of ParityCheck is

    signal Q: std_logic;
    signal D: std_logic;

begin

    D <= ParityCheck_data xor Q;
    Q <= '0' when ParityCheck_init = '1' else D when rising_edge(ParityCheck_clk);
    ParityCheck_err <= not Q;

end logicFunction;
```

A.7 ShiftRegister5

```
library ieee;
use ieee.std_logic_1164.all;

entity ShiftRegister5 is
    port(

        -- input
        ShiftRegister5_Reset: in std_logic;
        ShiftRegister5_data: in std_logic;
        ShiftRegister5_clk: in std_logic;
        ShiftRegister5_enableShift: in std_logic;

        -- output
        ShiftRegister5_D: out std_logic_vector(4 downto 0)

    );
end ShiftRegister5;

architecture logicFunction of ShiftRegister5 is

    signal D: std_logic_vector(4 downto 0);

begin

    D(4) <= '0' when ShiftRegister5_Reset = '1' else ShiftRegister5_data when rising_edge(ShiftRegister5_clk) and ShiftRegis
    D(3) <= '0' when ShiftRegister5_Reset = '1' else D(4) when rising_edge(ShiftRegister5_clk) and ShiftRegister5_enableShif
    D(2) <= '0' when ShiftRegister5_Reset = '1' else D(3) when rising_edge(ShiftRegister5_clk) and ShiftRegister5_enableShif
    D(1) <= '0' when ShiftRegister5_Reset = '1' else D(2) when rising_edge(ShiftRegister5_clk) and ShiftRegister5_enableShif
    D(0) <= '0' when ShiftRegister5_Reset = '1' else D(1) when rising_edge(ShiftRegister5_clk) and ShiftRegister5_enableShif

    ShiftRegister5_D <= D;

end logicFunction;
```

A.8 Counter3

```
library ieee;
use ieee.std_logic_1164.all;

entity Counter3 is
    port(

        -- input
        Counter3_CE: in std_logic;
        Counter3_CLK: in std_logic;
        Counter3_Reset: in std_logic;

        -- output
        Counter3_Q: out std_logic_vector(2 downto 0)

    );
end Counter3;

architecture logicFunction of Counter3 is

    component Adder3 is
        port(

            -- input
            Adder3_Ci: in std_logic;
            Adder3_A: in std_logic_vector(2 downto 0);
            Adder3_B: in std_logic_vector(2 downto 0);

            -- output
            Adder3_Co: out std_logic;
            Adder3_S: out std_logic_vector(2 downto 0)

        );
    end component;

    component Reg3 is
        port(

            -- input
            Reg3_In: in std_logic_vector(2 downto 0);
            Reg3_CE: in std_logic;
            Reg3_CLK: in std_logic;
            Reg3_Reset: in std_logic;

            -- output
            Reg3_Out: out std_logic_vector(2 downto 0)

        );
    end component;

    signal Q: std_logic_vector(2 downto 0);
    signal Adder3_S_to_Reg3_In: std_logic_vector(2 downto 0);

begin

    u0: Adder3 port map (
        Adder3_Ci => '0',
        Adder3_A => Q,
        Adder3_B => "001",
        Adder3_S => Adder3_S_to_Reg3_In
    );
```

```
u1: Reg3 port map (  
    Reg3_In => Adder3_S_to_Reg3_In,  
    Reg3_CE => Counter3_CE,  
    Reg3_CLK => Counter3_CLK,  
    Reg3_Reset => Counter3_Reset,  
    Reg3_Out => Q  
);  
  
Counter3_Q <= Q;  
  
end logicFunction;
```


A.9 Adder3

```
library ieee;
use ieee.std_logic_1164.all;

entity Adder3 is
    port(

        -- input
        Adder3_Ci: in std_logic;
        Adder3_A: in std_logic_vector(2 downto 0);
        Adder3_B: in std_logic_vector(2 downto 0);

        -- output
        Adder3_Co: out std_logic;
        Adder3_S: out std_logic_vector(2 downto 0)

    );
end Adder3;

architecture logicFunction of Adder3 is

    component FullAdder is
        port(

            -- input
            FullAdder_A: in std_logic;
            FullAdder_B: in std_logic;
            FullAdder_Ci: in std_logic;

            -- output
            FullAdder_S: out std_logic;
            FullAdder_Co: out std_logic

        );
    end component;

    signal c0_to_c1: std_logic;
    signal c1_to_c2: std_logic;

begin

    c0: FullAdder port map (
        FullAdder_A => Adder3_A(0),
        FullAdder_B => Adder3_B(0),
        FullAdder_Ci => Adder3_Ci,
        FullAdder_S => Adder3_S(0),
        FullAdder_Co => c0_to_c1
    );

    c1: FullAdder port map (
        FullAdder_A => Adder3_A(1),
        FullAdder_B => Adder3_B(1),
        FullAdder_Ci => c0_to_c1,
        FullAdder_S => Adder3_S(1),
        FullAdder_Co => c1_to_c2
    );

    c2: FullAdder port map (
        FullAdder_A => Adder3_A(2),
        FullAdder_B => Adder3_B(2),
        FullAdder_Ci => c1_to_c2,
        FullAdder_S => Adder3_S(2),
```

```
        FullAdder_Co => Adder3_Co
    );
end logicFunction;
```

A.10 Reg3

```
library ieee;
use ieee.std_logic_1164.all;

entity Reg3 is
  port(

    -- input
    Reg3_In: in std_logic_vector(2 downto 0);
    Reg3_CE: in std_logic;
    Reg3_CLK: in std_logic;
    Reg3_Reset: in std_logic;

    -- output
    Reg3_Out: out std_logic_vector(2 downto 0)

  );
end Reg3;

architecture logicFunction of Reg3 is
begin

  Reg3_Out(2) <= '0' when Reg3_Reset = '1' else Reg3_In(2) when rising_edge(Reg3_CLK) and Reg3_CE = '1';
  Reg3_Out(1) <= '0' when Reg3_Reset = '1' else Reg3_In(1) when rising_edge(Reg3_CLK) and Reg3_CE = '1';
  Reg3_Out(0) <= '0' when Reg3_Reset = '1' else Reg3_In(0) when rising_edge(Reg3_CLK) and Reg3_CE = '1';

end logicFunction;
```

A.11 FullAdder

```
library ieee;
use ieee.std_logic_1164.all;

entity FullAdder is
    port(

        -- input
        FullAdder_A: in std_logic;
        FullAdder_B: in std_logic;
        FullAdder_Ci: in std_logic;

        -- output
        FullAdder_S: out std_logic;
        FullAdder_Co: out std_logic

    );
end FullAdder;

architecture logicFunction of FullAdder is
begin

    FullAdder_S <= FullAdder_A xor FullAdder_B xor FullAdder_Ci;
    FullAdder_Co <= (FullAdder_A and FullAdder_B) or (FullAdder_Ci and (FullAdder_A xor FullAdder_B));

end logicFunction;
```

A.12 LCDDispatcher

```
library ieee;
use ieee.std_logic_1164.all;

entity LCDDispatcher is
    port(

        -- input
        LCDDispatcher_Reset: in std_logic;
        LCDDispatcher_Dval: in std_logic;
        LCDDispatcher_Din: in std_logic_vector(4 downto 0);
        LCDDispatcher_CLK: in std_logic;

        -- output
        LCDDispatcher_Wrl: out std_logic;
        LCDDispatcher_Dout: out std_logic_vector(4 downto 0);
        LCDDispatcher_done: out std_logic

    );
end LCDDispatcher;

architecture logicFunction of LCDDispatcher is

    component Counter5 is
        port(

            -- input
            Counter5_CE: in std_logic;
            Counter5_CLK: in std_logic;
            Counter5_Reset: in std_logic;

            -- output
            Counter5_Q: out std_logic_vector(4 downto 0)

        );
    end component;

    type Tstate is (wait_for_data, reset_counter, enable, cooldown, done);

    signal state: Tstate;
    signal next_state: Tstate;

    signal count_enable: std_logic;
    signal count_reset: std_logic;
    signal count_result: std_logic_vector(4 downto 0);

begin

    state <= wait_for_data when LCDDispatcher_Reset = '1' else next_state when rising_edge(LCDDispatcher_CLK);

    u0: Counter5 port map (
        Counter5_CE => count_enable,
        Counter5_CLK => LCDDispatcher_CLK,
        Counter5_Reset => count_reset,
        Counter5_Q => count_result
    );

    process(state, LCDDispatcher_Dval, LCDDispatcher_Din, count_result) begin

        case state is

            when wait_for_data =>
```



ISEL

Departamento de Engenharia
Eletrónica e Telecomunicações
e de Computadores

SLCDC (*Roulette Game*)

Laboratório de Informática e Computadores 2024 / 2025 verão

Autores: Ricardo Martins n^o52326 / Bernardo Silva n^o52605 / Bernardo Esteves n^o52948

```
        if LCDDispatcher_Dval = '1' then
            next_state <= reset_counter;
        else
            next_state <= wait_for_data;
        end if;

    when reset_counter =>
        next_state <= enable;

    when enable =>
        -- tw = 230ns  clk = 50mhz => min 12 ciclos (0b01100)
        if count_result = "01111" then
            next_state <= cooldown;
        else
            next_state <= enable;
        end if;

    when cooldown =>
        -- tc = 500ns  clk = 50mhz => min 25 ciclos (0b11001)
        -- if count_result(4) and count_result(3) and not count_result(2) and not count_result(1) and count_result(0)
        if count_result = "11111" then
            next_state <= done;
        else
            next_state <= cooldown;
        end if;

    when done =>
        if LCDDispatcher_Dval = '0' then
            next_state <= wait_for_data;
        else
            next_state <= done;
        end if;

    end case;
end process;

LCDDispatcher_Dout <= LCDDispatcher_Din;
count_enable <= '1' when state = enable or state = cooldown else '0';
count_reset <= '1' when state = reset_counter else '0';
LCDDispatcher_Wrl <= '1' when state = enable else '0';
LCDDispatcher_done <= '1' when state = done else '0';

end logicFunction;
```

B *Kotlin*

B.1 HAL

Algoritmo 1: HAL - Hardware Abstract Layer

```
import isel.leic.UsbPort

object HAL {

    /** ltimo _output_ enviado. */
    var lastOutput = 0

    /** Inicializa o _output_ do UsbPort. */
    fun init() = UsbPort.write(0)

    /** Verifica se os bits da `mask` est o ativos no _input_ do UsbPort. */
    fun isBit(mask: Int) = readBits(mask) == mask

    /** Retorna os bits no _input_ do UsbPort filtrados por `mask`. */
    fun readBits(mask: Int) = UsbPort.read() and mask

    /** Escreve no _output_ do UsbPort `value` filtrado por `mask`. */
    fun writeBits(mask: Int, value: Int) = write((value and mask) or (lastOutput and mask.inv()))

    /** Ativa no _output_ do UsbPort os bits da `mask`. */
    fun setBits(mask: Int) = write(lastOutput or mask)

    /** Desativa no _output_ do UsbPort os bits da `mask`. */
    fun clearBits(mask: Int) = write(lastOutput and mask.inv())

    /** Escreve no _output_ do UsbPort e guarda o que escreveu. */
    private fun write(output: Int){
        UsbPort.write(output)
        lastOutput = output
    }

}

fun main(){
    HAL.init()

    while(true){
        println(HAL.readBits(0xF).toString(2))
        readln()
    }
}
```

B.2 SerialEmitter

Algoritmo 2: SerialEmitter

```
import isel.leic.utils.Time

/** Envia tramas para os diferentes m dulos Serial Receiver */
object SerialEmitter {

  enum class Destination { LCD, ROULETTE }

  // [ NOTA IMPORTANTE! ]
  // 0 bits SEL t m que ser negados
  // Ou seja, para seleccionar o LCD, deve-se fazer HAL.clearBits(LCD_SEL)

  private const val LCD_SEL = 0b00000001
  private const val RD_SEL  = 0b00000010

  private const val SDX      = 0b00001000
  private const val SCLK     = 0b00010000

  /** Inicializa o SerialEmitter */
  fun init(){
    HAL.writeBits(
      LCD_SEL or RD_SEL or SDX or SCLK,
      LCD_SEL or RD_SEL // SDX e SCLK devem estar a zero
    )
  }

  /**
   * Envia uma trama para o _Serial Receiver_.
   * @property addr Destino
   * @property data Bits de dados
   * @property size N de bits a enviar
   */
  fun send(addr: Destination, data: Int, size: Int){

    // Ativar destino
    HAL.clearBits(when(addr){
      Destination.LCD -> LCD_SEL
      Destination.ROULETTE -> RD_SEL
    })

    // Enviar dados
    repeat(size){ i ->

      // Preparar SDX
      when((data shr i) and 1){
        1 -> HAL.setBits(SDX)
        0 -> HAL.clearBits(SDX)
      }

      // CLK
      HAL.setBits(SCLK)
      HAL.clearBits(SCLK)

    }

    // Enviar bit de paridade
    when(data.countOneBits() % 2){
      1 -> HAL.clearBits(SDX)
      0 -> HAL.setBits(SDX)
    }

    // CLK
    HAL.setBits(SCLK)
    HAL.clearBits(SCLK)

    // Desativar destino
    HAL.setBits(LCD_SEL or RD_SEL)
  }
}
```



```
fun main(){

    SerialEmitter.init()

    while(true){
        SerialEmitter.send(SerialEmitter.Destination.ROULETTE, readln().toInt(2), 8)
    }

    // println("11100001 - Off")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b11100001, 8)
    // Time.sleep(1000)
    //
    // println("11100000 - On")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b11100000, 8)
    // Time.sleep(1000)
    //
    // // clear
    //
    // println("00011111 - clear digit 0")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b00011111, 8)
    // Time.sleep(1000)
    //
    // println("00111111 - clear digit 1")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b00111111, 8)
    // Time.sleep(1000)
    //
    // println("01011111 - clear digit 2")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b01011111, 8)
    // Time.sleep(1000)
    //
    // println("01111111 - clear digit 3")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b01111111, 8)
    // Time.sleep(1000)
    //
    // println("10011111 - clear digit 4")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b10011111, 8)
    // Time.sleep(1000)
    //
    // println("10111111 - clear digit 5")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b10111111, 8)
    // Time.sleep(1000)
    //
    // // end clear
    //
    // println("00000000 - update digit")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b00000000, 8)
    // Time.sleep(1000)
    //
    // println("11000000 - update")
    // SerialEmitter.send(SerialEmitter.Destination.ROULETTE, 0b11000000, 8)
    // Time.sleep(1000)

    // 0 DXval n o parece ser ativo na simula o
    // Mas isso n o significa que n o est a funcionar
}
```

B.3 LCD

Algoritmo 3: LCD

```
import isel.leic.utils.Time

/** Escreve no LCD usando a interface a 4 bits. */
object LCD {

    // Dimens o do display.
    const val LINES = 2
    const val COLS = 16

    /** Define se a interface e S rie ou Paralela */
    private const val SERIAL_INTERFACE = true

    private const val RS_MASK = 0b010000
    private const val E_MASK = 0b100000

    private const val CGRAM_MASK = 0b01000000

    /** Escreve um nibble de comando/dados no LCD em paralelo. */
    private fun writeNibbleParallel(rs: Boolean, data: Int){

        if(rs) HAL.setBits(RS_MASK)
        else HAL.clearBits(RS_MASK)

        HAL.setBits(E_MASK)
        HAL.writeBits(0xF, data)
        HAL.clearBits(E_MASK)
    }

    /** Escreve um nibble de comando/dados no LCD em s rie. */
    private fun writeNibbleSerial(rs: Boolean, data: Int){

        // Adicionar bit de RS
        var data = data shl 1
        if(rs) data = data or 1

        SerialEmitter.send(SerialEmitter.Destination.LCD, data, 5)
    }

    /** Escreve um nibble de comando/dados no LCD. */
    private fun writeNibble(rs: Boolean, data: Int){
        require(data in 0x0..0xF){ "0x${data.toString(16)} is not a valid nibble" }
        return when(SERIAL_INTERFACE){
            true -> writeNibbleSerial(rs, data)
            false -> writeNibbleParallel(rs, data)
        }
    }

    /** Escreve um byte de comando/dados no LCD. */
    private fun writeByte(rs: Boolean, data: Int) {
        require(data in 0x00..0xFF){ "0x${data.toString(16)} is not a valid byte" }
        writeNibble(rs, data shr 4)
        writeNibble(rs, data and 0xF)
    }

    /** Escreve um comando no LCD. */
    private fun writeCMD(data: Int) = writeByte(false, data)

    /** Escreve dados no LCD. */
    private fun writeDATA(data: Int) = writeByte(true, data)

    /** Envia a sequ ncia de inicia o para comunica o a 4 bits. */
    fun init(){

        Time.sleep(20)
        writeNibble(false, 0b0011)
        Time.sleep(5)
        writeNibble(false, 0b0011)
        Time.sleep(1)
        writeNibble(false, 0b0011)
    }
}
```

```

    Time.sleep(1)
    writeNibble(false, 0b0010)

    writeCMD(0b00101000) // function set - DL=0 N=1 F=0
    Time.sleep(1)
    writeCMD(0b00001000) // display off - D=0 C=0 B=0
    Time.sleep(1)
    clear() // clear display
    Time.sleep(5)
    writeCMD(0b00000110) // entry mode set - I/D=1 S=0
    Time.sleep(1)
    writeCMD(0b00001100) // display on - D=1 C=0 B=0
}

/** Escreve uma string na posição corrente. */
fun write(text: String){
    for(c in text) write(c)
}

/** Escreve um carácter na posição corrente. */
fun write(char: Char) = writeDATA(char.code)

/** Envia um comando para posicionar o cursor. */
fun cursor(line: Int, column: Int){
    require(line in 0..LINES - 1) { "Line must be between 0 and ${LINES-1}" }
    require(column in 0..COLS - 1) { "Line must be between 0 and ${COLS-1}" }
    writeCMD(0b10000000 + line * 0x40 + column)
}

/** Envia comando para limpar o ecrã e posicionar o cursor na posição inicial. */
fun clear() = writeCMD(0b00000001)

/**
 * Regista um carácter personalizado.
 * @property char Carácter a associar.
 * @property picture Desenho do carácter 5x8.
 */
fun loadChar(char: Char, picture: List<String>){
    require(char.code in 0b000..0b111){ "Character is more than 3 bits" }
    repeat(8){ i ->
        writeCMD(CGRAM_MASK or (char.code shl 3) or i)
        val code = picture[i].map{ if(it == ' ') '0' else '1' }.joinToString("").toInt(2)
        writeDATA(code)
    }
    writeCMD(0b10)
}
}

fun main(){
    HAL.init()
    SerialEmitter.init()
    LCD.init()

    LCD.loadChar(0.toChar(), listOf(
        "UUUUU",
        "UUUUU",
        "U#U#U",
        "UUUUU",
        "#UUU#",
        "U##U",
        "UUUUU",
        "UUUUU"
    ))

    LCD.write("Hello!_${0.toChar()}")
    LCD.cursor(1, 0)
    LCD.write("0123456789")

    Time.sleep(3000)

    LCD.clear()

```

```
LCD.write("Goodbye...")  
  
Time.sleep(3000)  
  
LCD.clear()  
  
}
```

B.4 TUI

Algoritmo 4: TUI

```
import isel.leic.utils.Time
import util.Alignment

object TUI {

  /** 9+ - Para indicar que h mais de 9 cr ditos */
  const val NINE_PLUS = 0.toChar()

  /** Emoticon feliz - Para vit rias */
  const val HAPPY = 1.toChar()

  /** Emoticon triste - Para perdas */
  const val SAD = 2.toChar()

  /** S mbolo de Manuten o */
  const val MAINTENANCE = 3.toChar()

  /** Seta para a direita */
  const val ARROW = 4.toChar()

  /** Inicializa o TUI. */
  fun init(){

    LCD.clear()

    LCD.loadChar(NINE_PLUS, listOf(
      "###_ _",
      "#_ _ _",
      "###_ _",
      "_ _ _ _",
      "###_ _",
      "###_ _",
      "_ _ _ _",
      "_ _ _ _",
      "_ _ _ _"
    ))

    LCD.loadChar(HAPPY, listOf(
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _"
    ))

    LCD.loadChar(SAD, listOf(
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _"
    ))

    LCD.loadChar(MAINTENANCE, listOf(
      "#####",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _",
      " _ _ _ _"
    ))
  }
}
```

```

LCD.loadChar(ARROW, listOf(
    "UUUUU",
    "UU#UU",
    "UUU#U",
    "#####",
    "UUU#U",
    "UU#UU",
    "UUUUU",
    "UUUUU"
))

}

/* ----- LCD ----- */

/**
 * Escreve texto.
 * @property align Alinhamento.
 * @property range Limites do texto.
 */
fun write(text: String, line: Int, align: Alignment = Alignment.CENTER, range: IntRange = 0..LCD.COLS){
    require(line in 0 until LCD.LINES) { "Invalid line." }

    val rangeSize = range.last - range.start
    val startCol = range.start + when(align){
        Alignment.LEFT -> 0
        Alignment.CENTER -> (rangeSize - text.length) / 2
        Alignment.RIGHT -> rangeSize - text.length
    }

    updateLine(line, text, startCol)
}

/**
 * Atualiza a frame de anima o de um texto rotativo.
 *
 * til para mostrar texto maior do que a largura do LCD.
 */
fun scrollText(text: String, line: Int, speed: Int = 250, range: IntRange = 0..LCD.COLS){
    require(line in 0 until LCD.LINES) { "Invalid line." }

    val time = Time.getTimeInMillis() / speed
    val rangeSize = range.last - range.start

    val text = "$text" // Adicionar espaço como margem
    var res = text.substring((time % text.length).toInt()) // Cortar texto
    while(res.length < rangeSize) res += text // Duplicar texto para ocupar espaço inteiro
    res = res.substring(0 until rangeSize) // Manter texto dentro do range

    updateLine(line, res, range.start)
}

fun clear(){
    line0 = List(LCD.COLS){ " " }.joinToString("")
    line1 = List(LCD.COLS){ " " }.joinToString("")
    LCD.clear()
}

private var line0 = List(LCD.COLS){ " " }.joinToString("")
private var line1 = List(LCD.COLS){ " " }.joinToString("")

/** Atualiza as linhas do LCD evitando comandos redundantes. */
private fun updateLine(line: Int, text: String, start: Int = 0){
    // Obter último estado da linha
    val lastLine = when(line){
        0 -> line0
        1 -> line1
        else -> throw IllegalArgumentException("Invalid line.")
    }

    // Sobrescrever linha

```

```

val prefix = if(start > 0) lastLine.substring(0 until start) else ""
val suffix = if(start + text.length <= LCD.COLS) lastLine.substring(start + text.length) else ""
val currLine = (prefix + text + suffix).substring(0 until LCD.COLS)

// Ignorar se n o existir altera es
if(lastLine == currLine) return

// Escrever caract res nos locais necess rios
var col: Int? = null
repeat(LCD.COLS){ i ->
    if(lastLine[i] == currLine[i]) return@repeat

    if(col != i) LCD.cursor(line , i)
    LCD.write(currLine[i])
    col = (col ?: 0) + 1
}

// Atualizar ltime estado da linha
when(line){
    0 -> line0 = currLine
    1 -> line1 = currLine
}

}

/* ----- Keyboard ----- */

/** Retorna de imediato a tecla premida ou `NONE` se n o h tecla premida. */
fun getKey() = KBD.getKey()

}

fun main(){

    HAL.init()
    SerialEmitter.init()
    LCD.init()
    TUI.init()

    while(true){

        TUI.scrollText("If you are seeing this text scrolling , it means that the TUI is working!", 0)

        val key = TUI.getKey()
        if(key != 0.toChar()) TUI.write(key.toString(), 1)

    }

}

```